

---


# EECS 16A    Designing Information Devices and Systems I

## Spring 2022    Discussion 8A

---
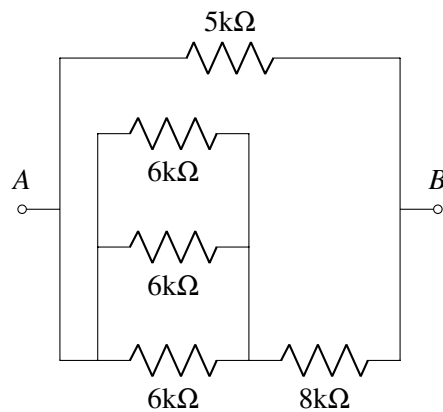
### 1. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals  $A$  and  $B$  using the resistor combination rules for series and parallel resistors.




### 2. Superposition


For the following circuits:

- i. Use the superposition theorem to solve for the voltages across the resistors. First, redraw the circuits with just one source (while zero-ing the other source). Then, for each circuit solve for each element voltage. Finally, sum the voltages at each node.


(a)

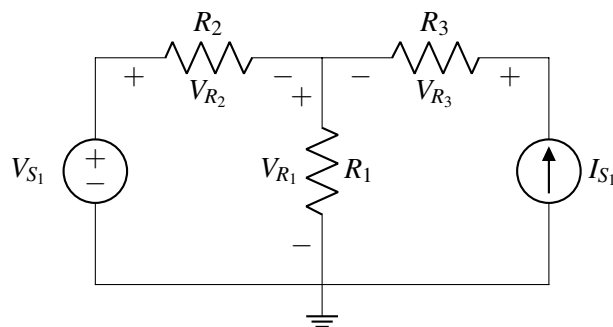

(b)


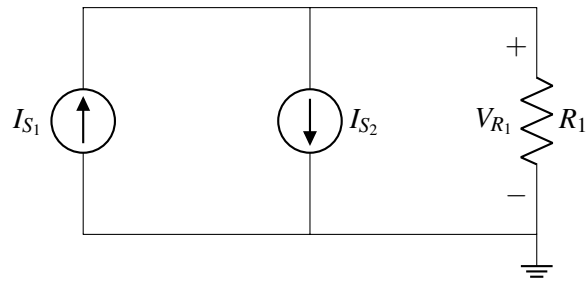


(c) (PRACTICE)

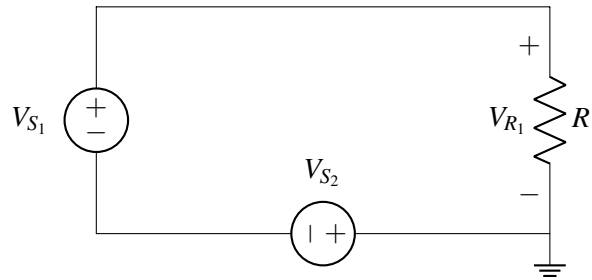
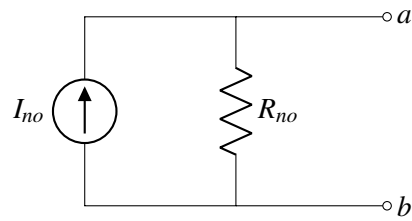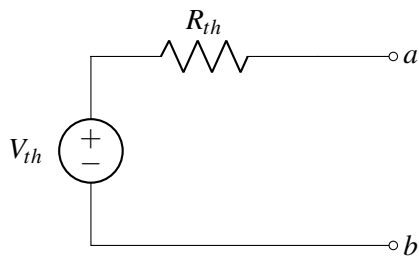
### 3. Thevenin and Norton Equivalence

The general Thévenin and Norton equivalents are shown below:



Find the Thévenin and Norton equivalents across terminals  $a$  and  $b$  for the circuit given below.

