

---

EECS 16A    Designing Information Devices and Systems I    Homework 10  
 Spring 2022

---

**This homework is due April 8, 2022, at 23:59.**

**Self-grades are due April 11, 2022, at 23:59.**

**Submission Format**

Your homework submission should consist of **one** file.

- `hw10.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

Submit the file to the appropriate assignment on Gradescope.

**1. Reading Assignment**

**No submission is required for this problem, however we ask that you read and understand the notes.**

For this homework, please read Note 17A to learn about comparators and op-amps, and Note 17B to learn about charge sharing. You are always encouraged to read beyond this as well.

- If the op-amp supply voltages are  $V_{DD} = 5\text{ V}$  and  $V_{SS} = 0\text{ V}$ , then what is the minimum/maximum value of  $V_{out}$ ?
- What is the purpose of a comparator? How can we use a comparator circuit to detect a touch for a capacitive touchscreen?

**2. Fun With Charge Sharing**

- Capacitors  $C_1$  and  $C_2$  are charged to  $V_1$  and  $V_2$  and switch  $S_1$  is open for time  $t < 0$ . At time  $t = 0$ , switch  $S_1$  is closed. Calculate  $V_1$  at time  $t > 0$ .


 


Figure 1: Capacitor Charge Sharing

Use the following values:  $C_1 = 1\text{ F}$ ,  $C_2 = 4\text{ F}$ ,  $V_1 = 6\text{ V}$ ,  $V_2 = 1\text{ V}$ .

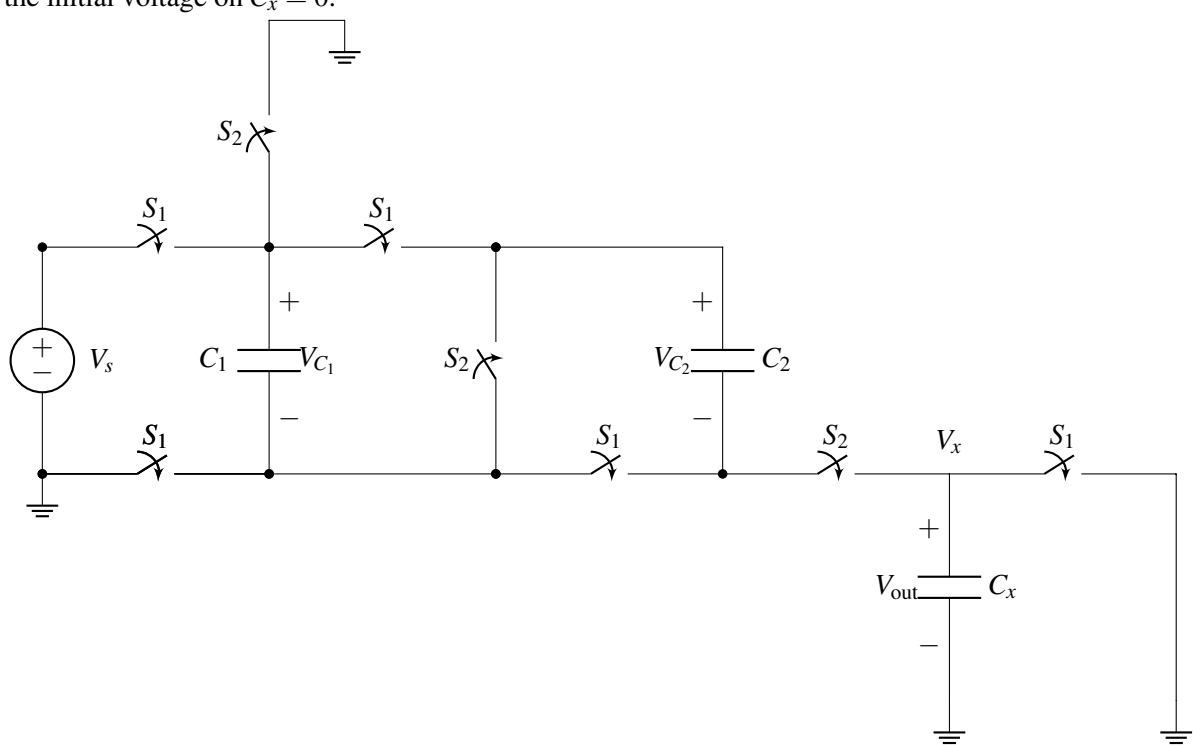
(b) The circuit shown below operates in two phases. During phase 1, switches labeled  $S_1$  are closed and switches  $S_2$  are open. During phase 2, switches  $S_1$  are open and switches  $S_2$  are closed. Assume that the initial voltage on  $C_x = 0$ .



- i. Redraw the circuit during phase 1. Replace closed switches with "wires" and open switches with "open circuits" (i.e. just omit them from the diagram). Use  $C_1 = C_2 = C_0$ .
- ii. Redraw the circuit during phase 2. Replace closed switches with "wires" and open switches with "open circuits" (i.e. just omit them from the diagram). Use  $C_1 = C_2 = C_0$ .
- iii. Calculate the value of the voltage  $V_{out}$  during phase 2 as a function of  $C_0$ ,  $C_x$ , and  $V_s$ . Use  $C_1 = C_2 = C_0$ .
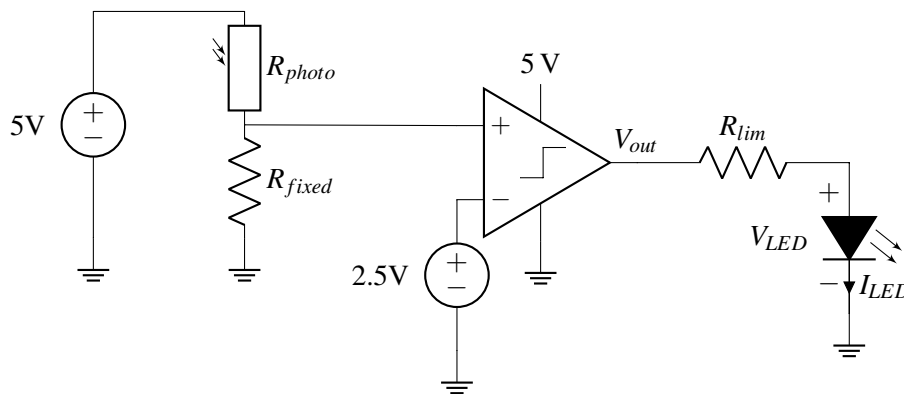
### 3. LED Alarm Circuit

One day, you come back to your dorm to find that your favorite candy has been stolen. Determined to catch the perpetrator red-handed, you decide to put the candy inside a kitchen drawer. Using the following circuit design, you would like to turn on a light-emitting diode (LED) "alarm" if the kitchen drawer is opened.



Note  $R_{photo}$  is a photoresistor, which acts like a typical resistor but changes resistance based on the amount of light it is exposed to. This photoresistor is located inside the kitchen drawer, so we can tell when the drawer is opened or closed.

$V_{LED}$  indicates the voltage across the LED; we will guide you through the IV behavior of this element later in the problem. The LED is located in your room (and connected to a long wire going to the kitchen), so that you can remotely tell when the kitchen drawer has been opened.

(a) What is  $V_+$ , the voltage at the positive voltage input of the comparator? Your answer should be written in terms of  $R_{photo}$  and  $R_{fixed}$ .

(b) We now want to choose a value for  $R_{fixed}$ . From the photoresistor's datasheet, we see the resistance in "light" conditions (i.e. drawer open) is  $1\text{ k}\Omega$ . In "dark" conditions (i.e. drawer closed), the resistance is  $10\text{ k}\Omega$ .

To ensure the comparator detects the light condition with more tolerance, we decide to design  $R_{fixed}$  so that  $V_+$  is  $3\text{ V}$  under the "light" condition. Solve for the value of  $R_{fixed}$  to meet this specification.

(c) Write down  $V_{out}$  with any conditions in terms of  $V_+$ . For simplicity, consider the case when  $V_+ \neq V_-$  and assume the comparator is ideal.


(d) Using your answers to the previous parts, write down  $V_{out}$  with the conditions on its output in terms of  $R_{photo}$ . You can substitute the value of  $R_{fixed}$  you found in part (b). As before, you can assume that  $V_+ \neq V_-$  and the comparator is ideal.

(e) From the design steps in the previous parts, we have designed a circuit that outputs non-zero voltage when the photoresistor is exposed to light (i.e. kitchen drawer open). We now want to design the LED portion of the circuit, so we get a visual alarm when the drawer is open.

From the LED's datasheet, the forward voltage,  $V_F$  is  $3\text{ V}$ . Essentially, if  $V_{LED}$  is less than this voltage, the LED won't light up and  $I_{LED}$  will be  $0\text{ A}$ .

Here is an idealized IV curve of this LED. The LED behaves in one of the following two modes:

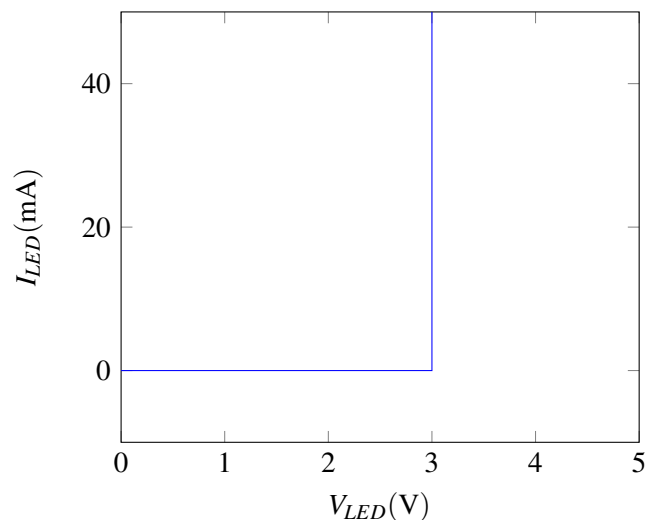- i. If the voltage across the LED is less than  $V_F = 3\text{ V}$  or if  $I_{LED} < 0\text{ A}$ , then the LED acts like an open circuit.
- ii. If the voltage across the LED is  $V_F = 3\text{ V}$ , then the LED acts like a voltage source, except that it only allows positive current flow (i.e. only in the direction of current marked on the circuit diagram).




To avoid exceeding the power rating of the LED (and having it burn out), the recommended value for  $I_{LED}$  is 20 mA.

Find the value of the current-limiting resistor,  $R_{lim}$ , such that when the photoresistor is in the “light” condition,  $I_{LED} = 20$  mA.
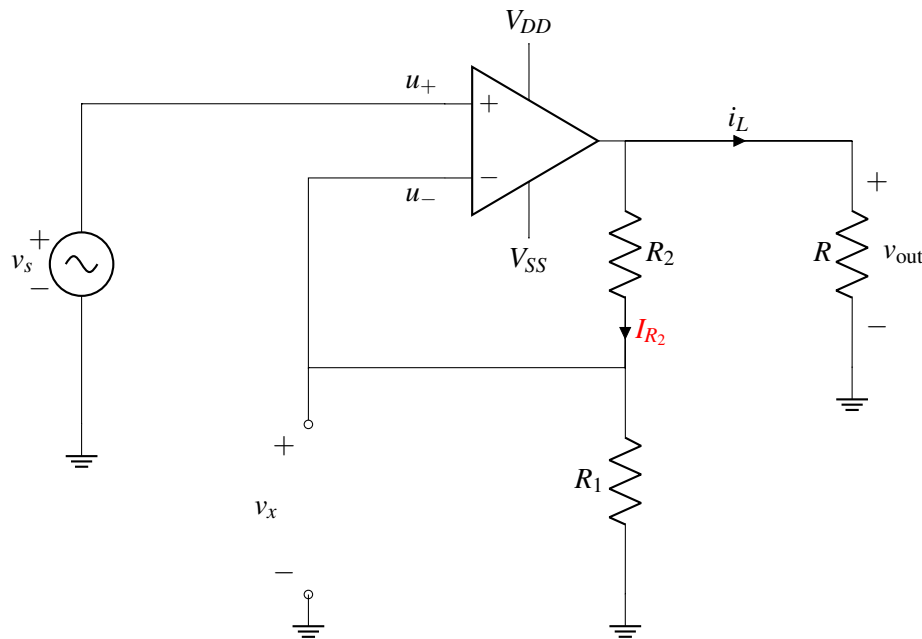
#### 4. Op-Amp in Negative Feedback

In this question, we analyze op-amp circuits that have finite op-amp gain  $A$ . We replace the op-amp with its circuit model with parameterized gain and observe the gain’s effect on terminal and output voltages as the gain approaches infinity. **Note here that  $V_{SS} = -V_{DD}$ .**



**For parts (a) - (e) only, assume that the op-amp is ideal (i.e.,  $A \rightarrow \infty$ ).** We will consider the case of finite gain  $A$  in parts (f) - (h).

- Consider the circuit shown above and  $V_{SS} = -V_{DD}$ . What is  $u_+ - u_-$ ?
- Find  $v_x$  as a function of  $v_{out}$ .
- What is  $I_{R_2}$ , i.e. the current flowing through  $R_2$  as a function of  $v_s$ ? *Hint: Find the current through  $R_1$  first.*
- Find  $v_{out}$  as a function of  $v_s$ .
- What is the current  $i_L$  through the load resistor  $R$ ? Give your answer in terms of  $v_{out}$ .

 


Figure 2: Op-amp model

- (f) We will now examine what happens when  $A$  is not  $\infty$ . To understand what happens in this case, first draw an equivalent circuit for the first op amp circuit, **by replacing the ideal op-amp in the non-inverting amplifier with the op-amp model shown above.**

Now, using this setup, calculate  $v_{out}$  and  $v_x$  in terms of  $A$ ,  $v_s$ ,  $R_1$ ,  $R_2$  and  $R$ . Is the magnitude of  $v_x$  larger or smaller than the magnitude of  $v_s$ ? Do these values depend on  $R$ ? *Hint: Note that the first golden rule still applies, i.e. the currents through the input terminals are zero.*


- (g) Using your solution to the previous part, calculate the limits of  $v_{out}$  and  $v_x$  as  $A \rightarrow \infty$ . You should get the same answer as in part (d) for  $v_{out}$ .
- (h) **[OPTIONAL, CHALLENGE]** Now you want to make a non-inverting amplifier circuit whose gain is nominally  $G_{nom} = \frac{v_{out}}{v_s} = 1 + \frac{R_2}{R_1} = 4$ . However,  $G_{nom}$  can only be achieved only if the op-amp is ideal, i.e, if its internal gain  $A \rightarrow \infty$ . But, as with most considerations in the physical world, we must account for nonidealities! In reality, because you will be working with an op-amp with finite gain  $A$ , your designed circuit gain may come close to but will never quite reach  $G_{nom}$  as a result of the real op-amp's finite internal gain  $A$ .

Suppose you would like your real op-amp circuit to have a maximum error of 1% (i.e, a minimum circuit gain of 3.96, i.e.  $\frac{v_{out}}{v_s} \geq 3.96$ ). Remember that only if your op-amp were ideal, you would have a nominal circuit gain of  $G_{nom} = \frac{v_{out}}{v_s} = 1 + \frac{R_2}{R_1} = 4$ .

What is the minimum required value of  $A$ , called  $A_{min}$ , to achieve that specification? *Hint: Use your expression of  $v_{out}$  in part (f) to find an expression for  $G_{min} = \frac{v_{out}}{v_s}$  when  $A \neq \infty$ .*
 
## 5. Op Amp Nodal Analysis

Consider this op amp circuit below. We are interested in analyzing its input-output relationship, finding the Thevenin equivalent of this op amp circuit, and making some observations about the resulting equivalent.



- What is the node voltage at  $u_1$ ?
- Write a KCL equation at node  $u_2$ .
- Write a KCL equation at node  $u_3$ .
- Write an expression relating voltages  $u_4$  and  $u_5$ .
- Noting that this circuit is in negative feedback and putting together every expression we have derived in previous parts, find an expression for  $V_{out}$  as a function of  $V_1$  and  $V_2$
- Turn off all independent sources ( $V_1 = V_2 = 0V$ ). What is the equivalent resistance as seen between terminals  $a$  and  $b$ ? This will be your Thevenin resistance,  $R_{Th}$ . (Hint: Consider what the voltage at the output of the op amp becomes and use a test source, or replace the op amp with its internal model where it has a dependent source.)
- Use what you found in parts  $b$  and  $c$  to draw the Thevenin equivalent.
- Practice (Optional)**: Does the Thevenin resistance depend on all the resistors or a strict subset? What might explain this?

## 6. Homework Process and Study Group

Who did you work with on this homework? List names and student ID's. (In case you met people at homework party or in office hours, you can also just describe the group.) How did you work on this homework? If you worked in your study group, explain what role each student played for the meetings this week.