
EECS 16A Touchscreen 3B

Insert your names here

Semester Outline



Imaging
Module



Touchscreen
Module



Acoustic
Positioning
Module

Announcements



- Touchscreen buffer will be held during the week of **4/11-4/15**
- Fill out the form at the end of the notebook if you plan to attend!
- Buffer lab is **not required** if you've completed Touch 1, Touch 2, Touch 3A, and Touch 3B

Announcements

- Optional touchscreen lab will also be held during the week of **4/11-4/15!**
- You'll build a capacitive touchscreen using charge sharing instead of integration
- Fill out the form at the end of the notebook if you plan to attend!

Last time: Touch 3A

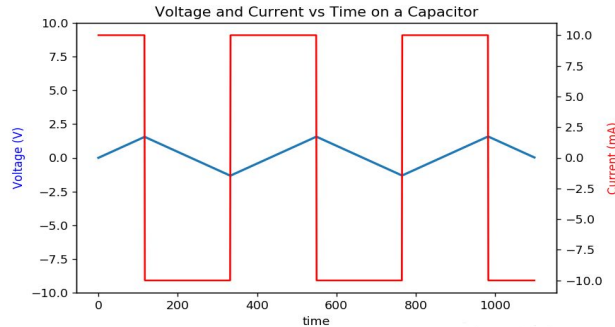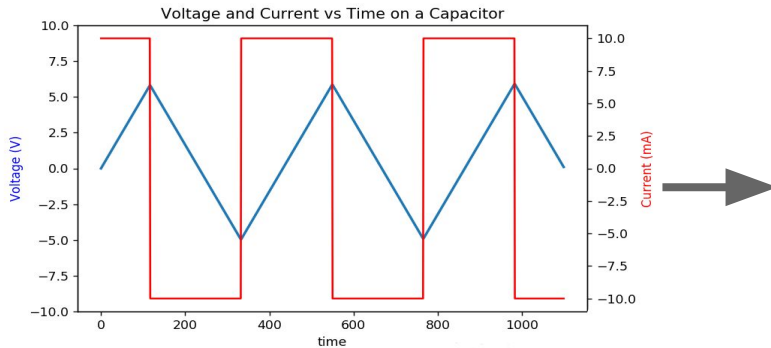- Simulated a touch-sensing circuit
 - Current source onto cap gave $V(t) = \frac{I}{C}t + V_0$
 - Periodically charging and discharging gives a triangular shaped waveform
- **What changed between touch and no touch?**
 - Can see this change with a comparator!



Last time: Touch 3A


- We plan to use a comparator to actuate an LED
- Problem: we don't have ideal square current sources
 - Need another way to implement last lab's waveforms (the triangle wave output)
 - How do we go about creating a similar system that still fits our model?

This week: Touch 3B

- Explore an alternative to ideal current sources
 - Use our new (and proven) op amp skills
- Build a complete system that will detect touch and actuation

Electronic Systems: A review

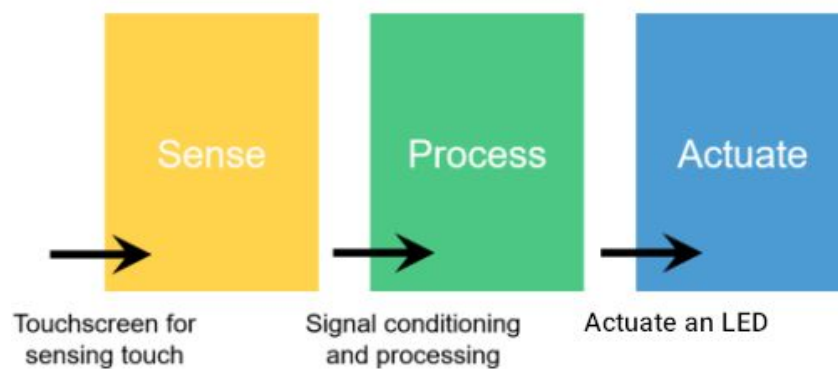- Sensing is only a part of a complete system. Most systems perform 3 tasks:
 - Sense (Physical to Electrical)
 - Process (Signal Conditioning)
 - Actuate (Electrical to Physical)





Building a current source (Note 20)

- Need a circuit that outputs a constant current regardless of voltage across
- What we have:
 - Voltage sources
 - $V = IR$ relationship for resistors
 - Note 20's guidance


First attempt at a current source

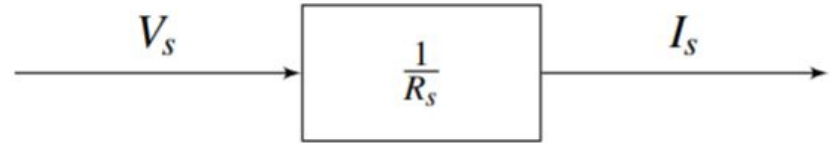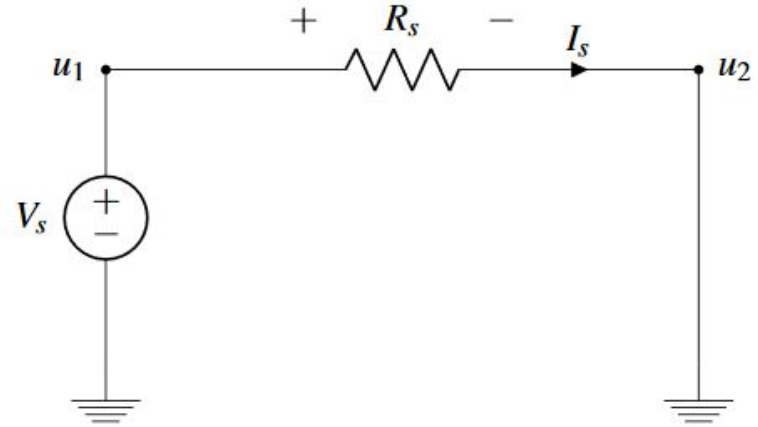- If we have a voltage source and a resistor then we can create a “current source”
- The current is just $(V_s - 0)/R_s$ since the other side is $0V$



First attempt evaluation

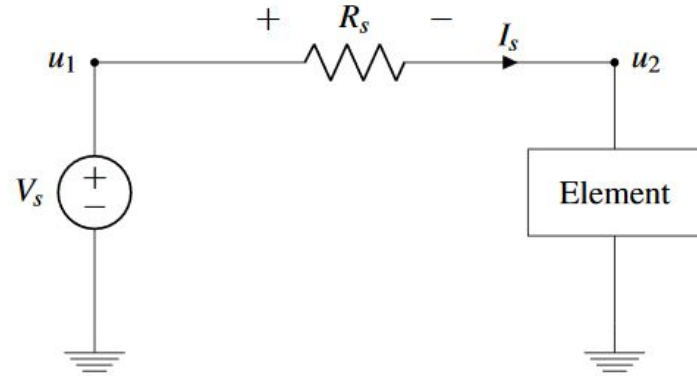- What happens when we attach a load?
- Assume that the element is a resistor of value R_L
- **Does this work?**




NOPE, it changes the current

$$I_s = \frac{V_s}{R_S + R_L}$$


Try again

- The issue here is that we had $I_s = \frac{V_s - 0}{R_s}$
- But a load made it so R_s isn't connected to 0 on the other side
- We need to set the u_2 node voltage to 0 for this to work
- **Do you know anything that can force nodes to 0V?**

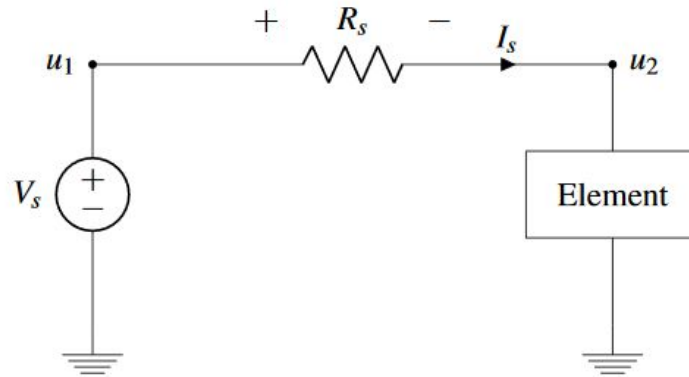


Note 20: An “almost” current source

- We can use an op amp!
 - GR #1: No current going in to op amp
 - GR #2: $U_+ = U_-$, so let's make one of them 0V
 - **What must be true for this to hold?**

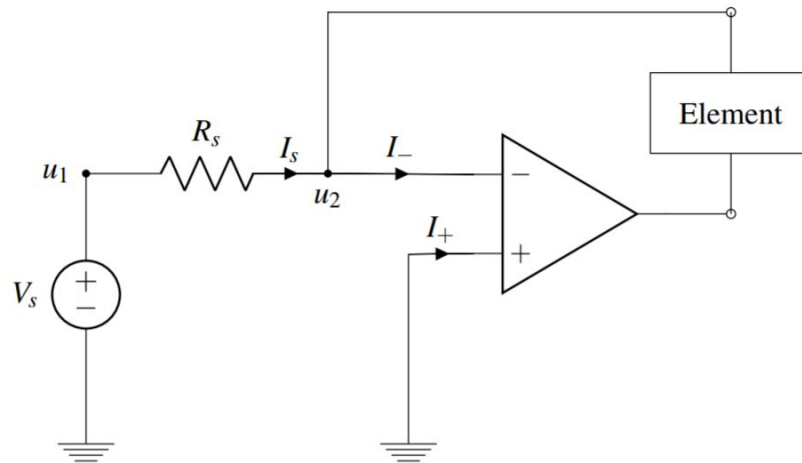



Note 20: An “almost” current source

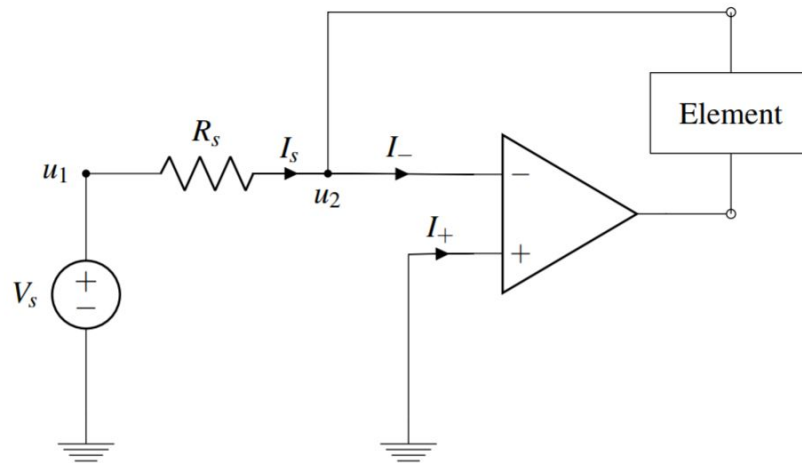- Since we are in negative feedback, $u_2 = 0V$
 - $I_s = \frac{V_s - 0}{R_s}$
- All current will go to the element, since $I_- = 0$



Sensing a completion

- Hook up our capacitive touch screen
- We get a constant current through the capacitor
- **What's the output of this circuit?**

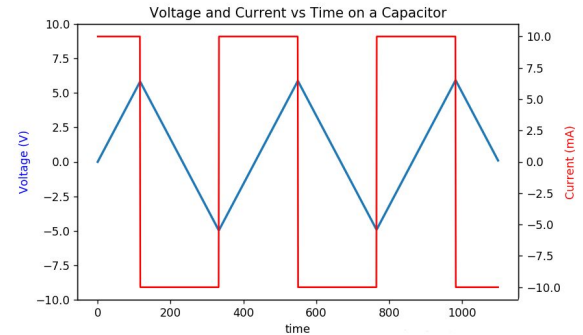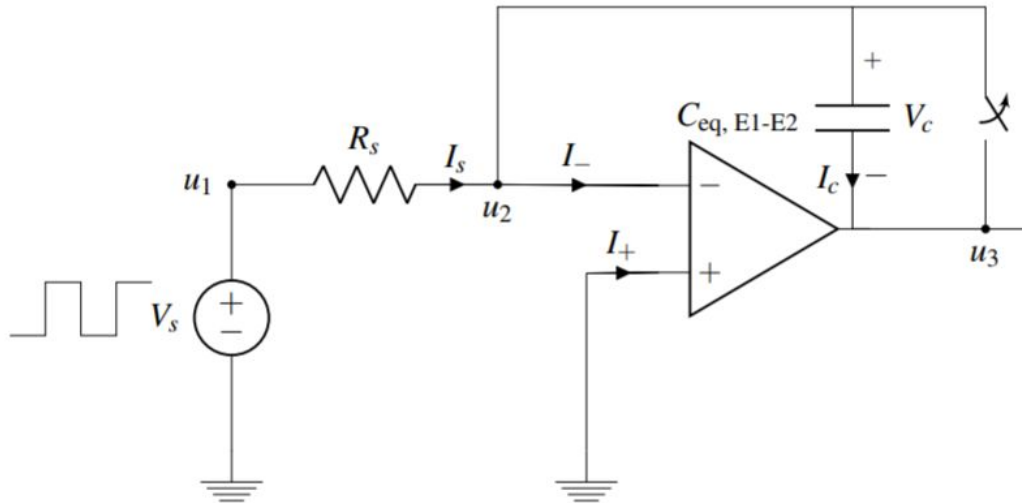

Note 20: An “almost” current source

- Constant current is cool, but we want periodic current to discharge the cap.
- What if we periodically switch voltage?

$$I_S = \frac{V_s}{R} \longrightarrow I_S = \frac{-V_s}{R}$$

An alternate viewpoint

- Note that the output of this circuit is
- It's also an integral, just like last time.
 - New circuit is an “almost current source” or just trading current for voltage.
- We're now integrating a constant voltage instead of a current, but the net result is the same as last time
- *We traded one type of input for another!*
- *Variable voltage sources do exist, so this is good!*
What are they like though?

$$V_{out} = -\frac{1}{R_s C} \int_0^t V_s dt$$


What's our new input?

- Function generator
- Can create different waves
- Treat it as a non-constant voltage source
- Now we can make the “almost current source” of our dreams!




Processing the rest of our system

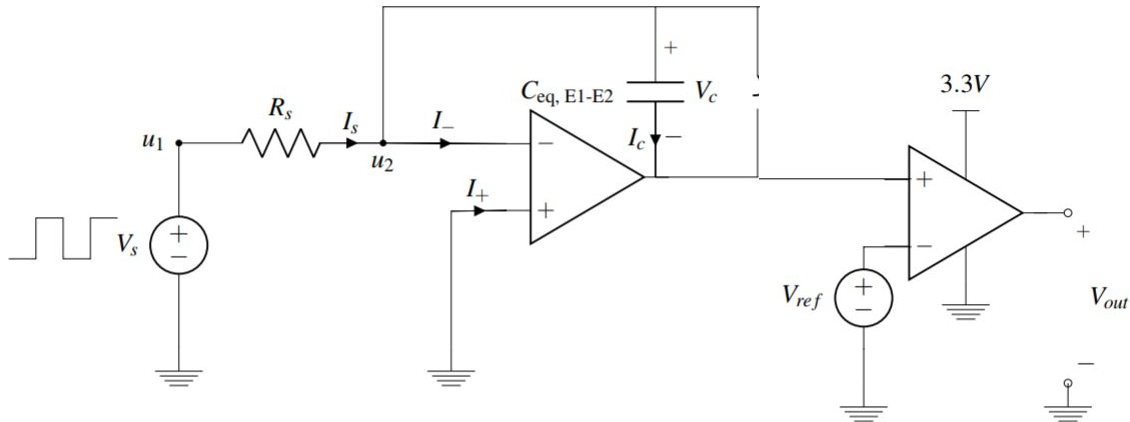
- Our circuit behaves as intended
- We can feed the new signal into our comparator circuit from last time



Our real-world circuit

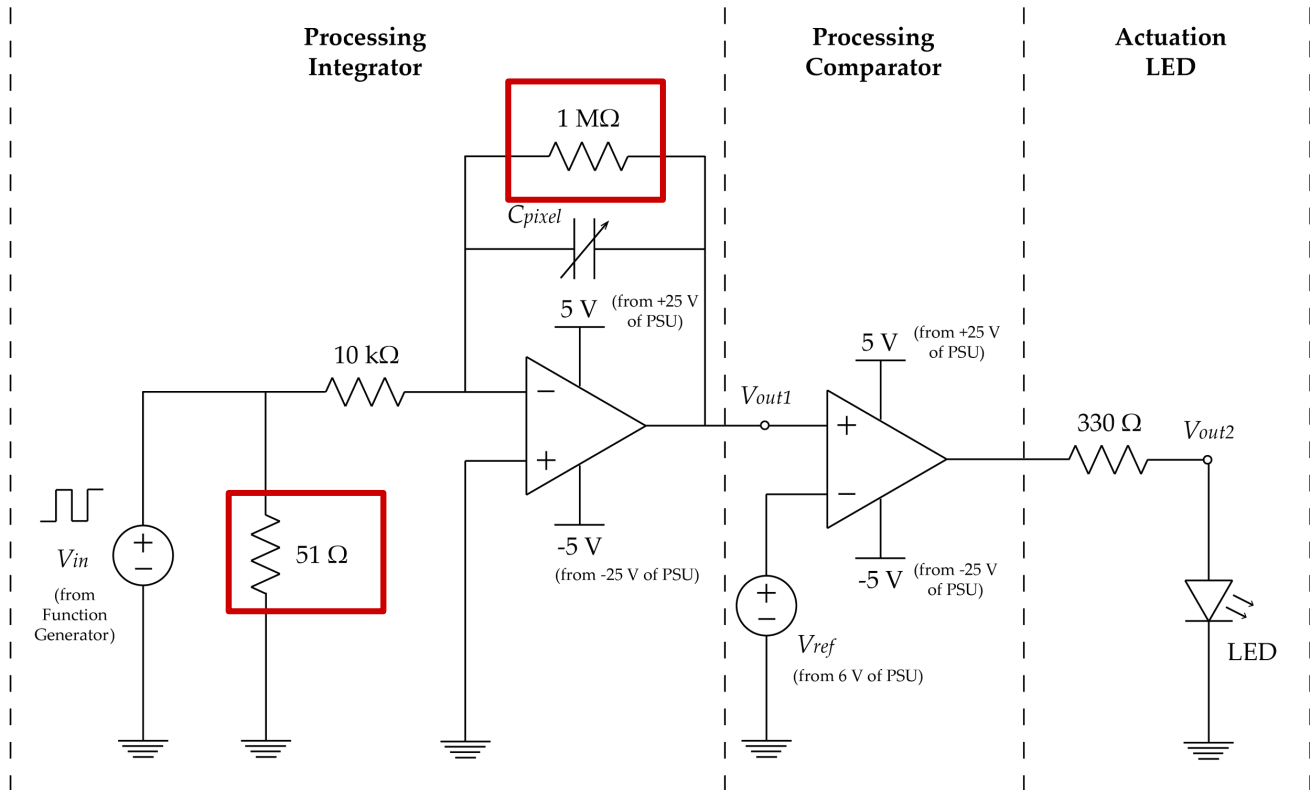


Our real-world circuit

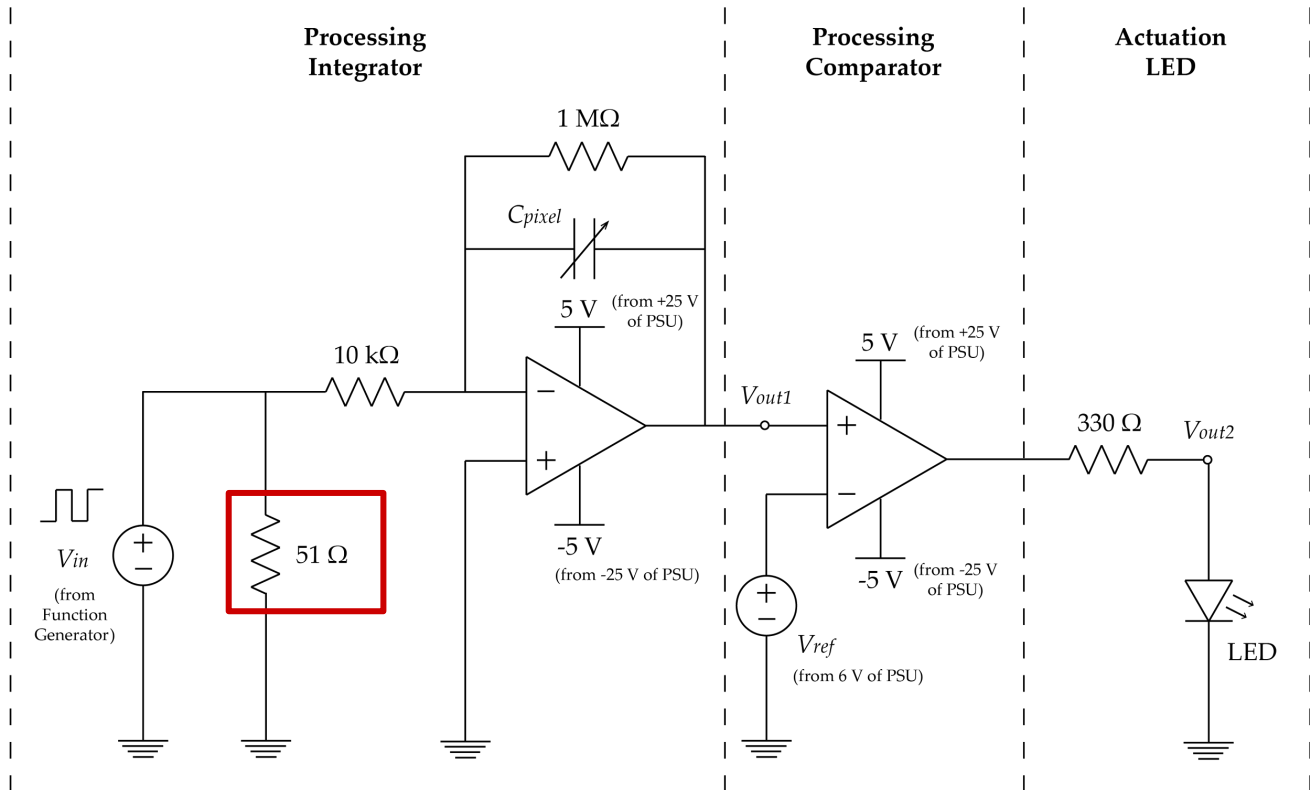

Note: Voltage dividers


- The function generator has a 50 Ohm source resistance
- Our function generator also assumes a 50 Ohm load is attached (just because).
 - **What's the voltage you get across this load?**

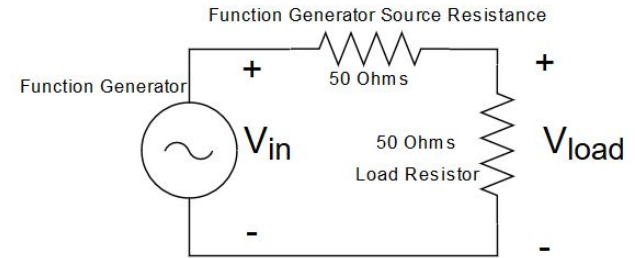If you attach a 50 Ohm load, then the load only gets $\frac{1}{2}$ of V_{in} applied




Note: Voltage dividers

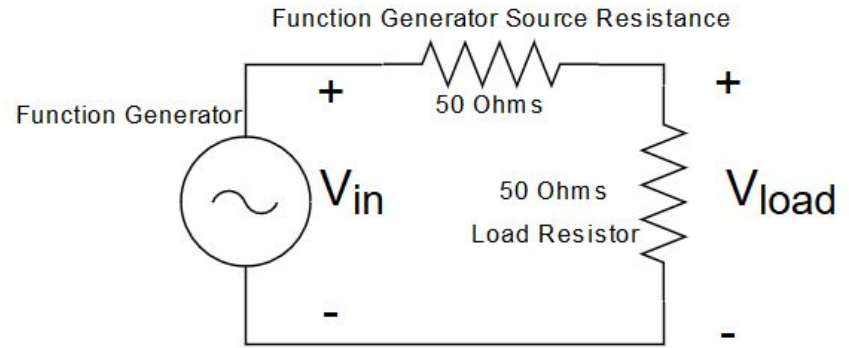- The function generator will automatically double its output voltage (V_{in}) so that the voltage across the load (V_{load}) is what you would expect after it is halved




What does the 51 ohm do?

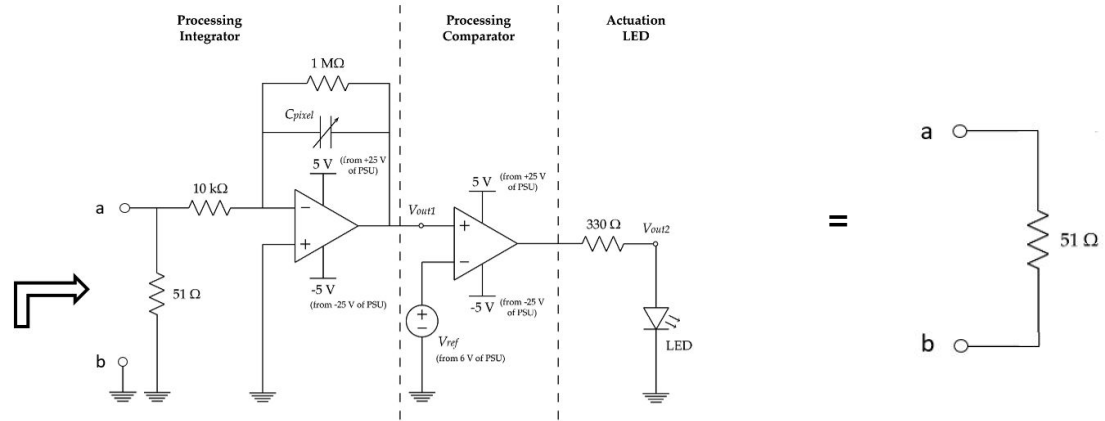- Compute the thevenin resistance of our circuit from the input port
 - It's about 51 Ohms
- Our circuit (from the input) looks like a 51 Ohm resistor




What does the 51 ohm do?

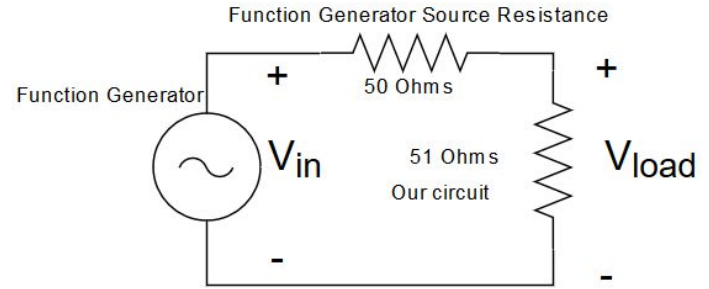- Our circuit looks like a 51 ohm load with respect to the input, so the function generator is happy!
- (Note: 50 Ohm resistors basically don't exist so we use 51 because it's the next closest value)



Our real-world circuit

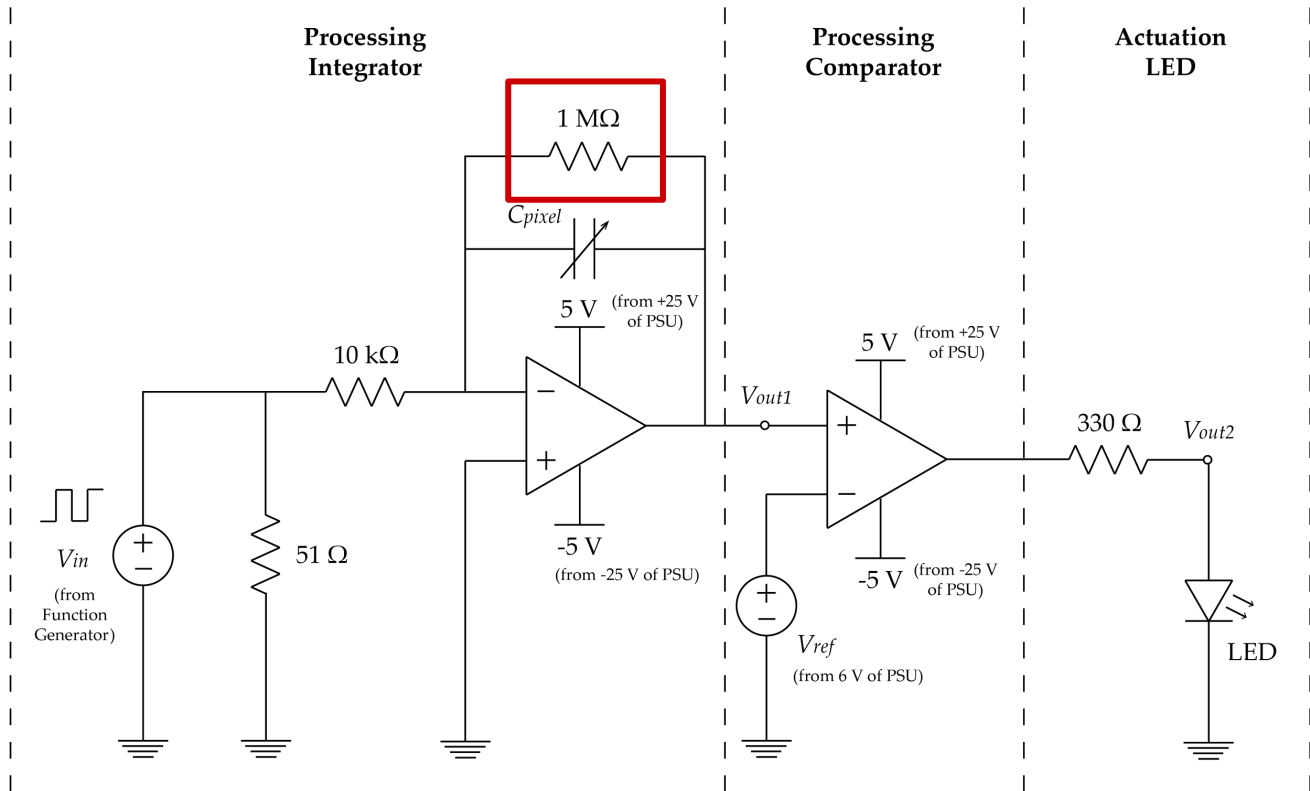

Another difference:

- It's a little out of scope
- It ensures that the circuit is always in negative feedback
 - Since it's 1 million Ohms it draws almost 0 current, and thus doesn't really affect our analysis
- If it was not there, the Capacitor acts as an open during constant voltage, so there is no feedback

Taking the limit

- Didn't you say capacitive touchscreen is way better than resistive? Why do we only have one touch point instead of nine?


Taking the limit

- Note that this isn't dependent on voltage dividers at all, only on if you are locally touching the capacitor
- **How to add more touch points?**
 - Duplicate the entire circuit and put them next to each other. Each one is a pixel
- They're independent, so the more you add the more points you can sense

Taking the limit

- Make the caps really small, put them in the size of a screen
- Thousands of these sensing circuits can be made incredibly small
 - (less than 4mm x 4mm)
- Put a thousand of these and you can recognize 1000 different touch points
- No moving parts, much better (and more accurate) than the resistive touchscreen


That's it!

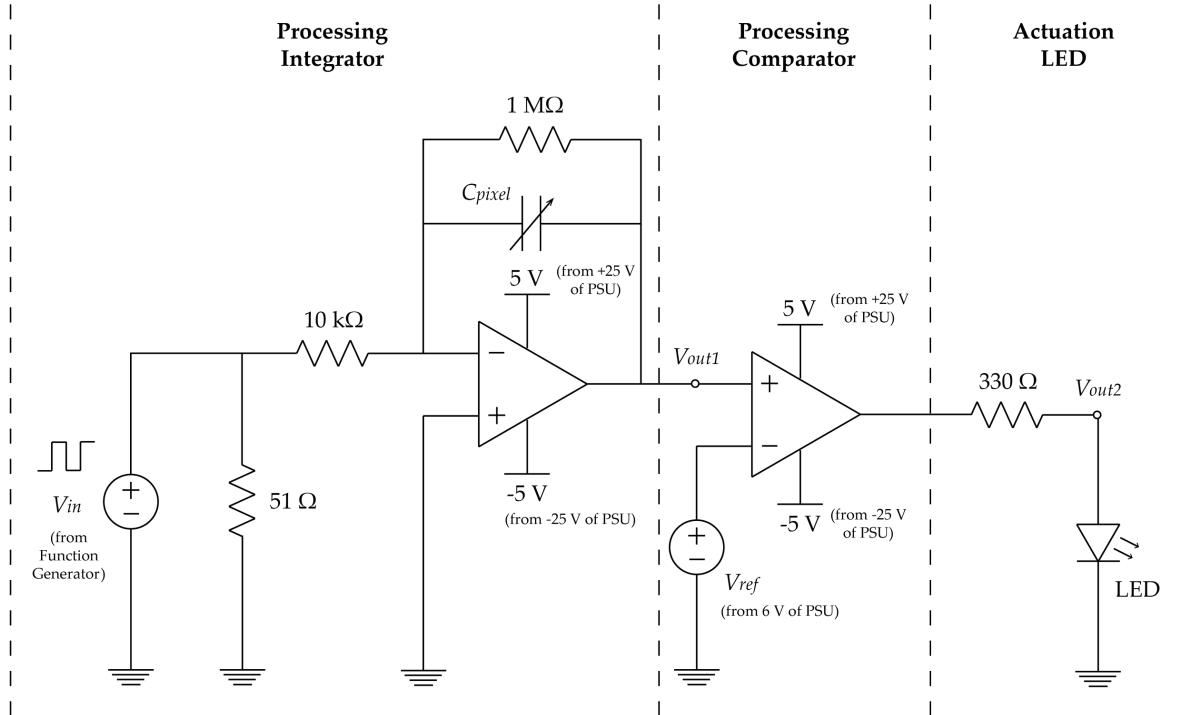

Quick note

- Planar wiring **required**
- We can and will refuse to help you fix your circuit if it's too messy
 - Use the breadboarding wires at the TA desk and the wire strippers at your stations
 - Cut wires and resistors to be as short as you can and have them still work.

Why is planar wiring required?

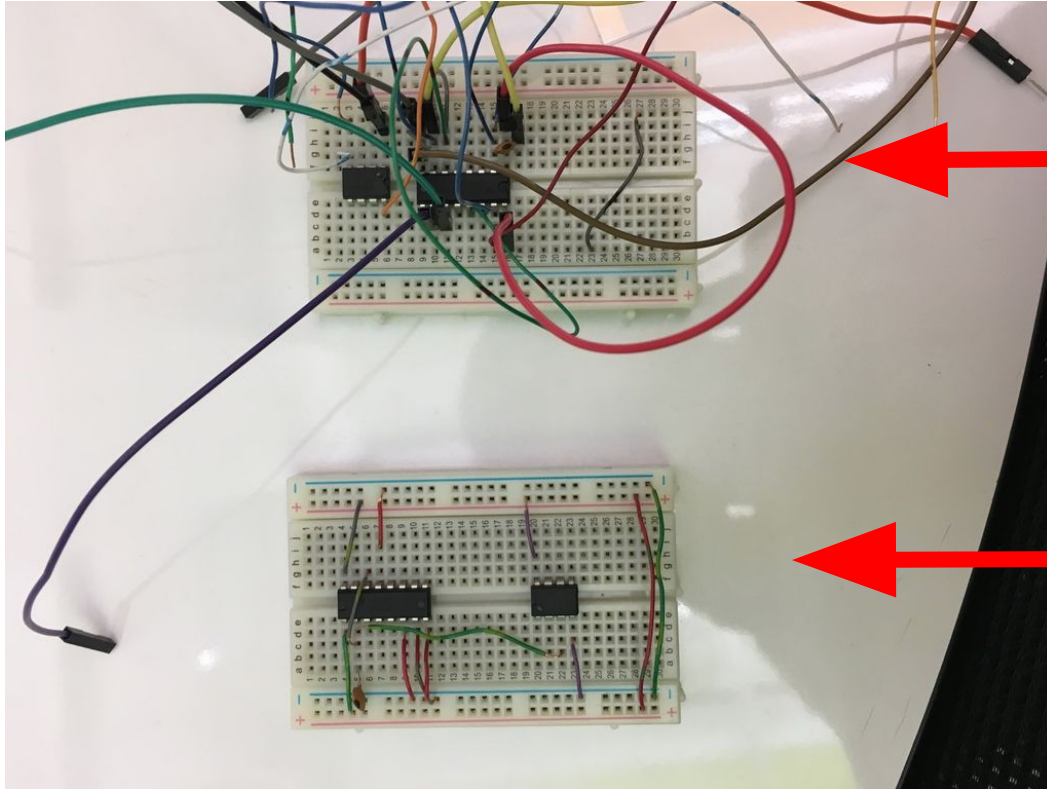


1.5 Hour to debug;
Falls apart easily


5 seconds to debug;
Practically 2D;
Lasts a lifetime

Keep your circuits neat!

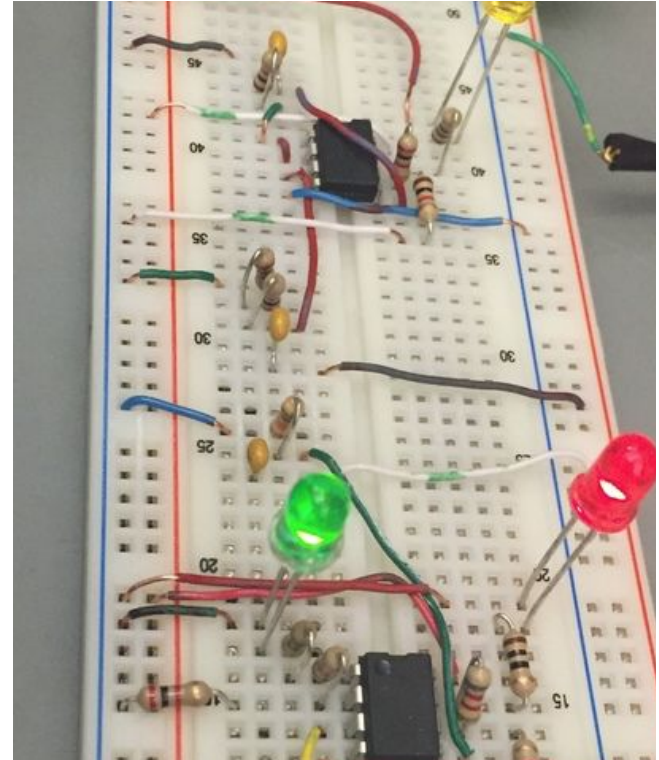- **Cut wires to correct lengths.**
- Place op amp across the middle of your breadboard (should already be there).
- If circuit is not neat, will not debug until it is.
- Get Started!



And that's it!

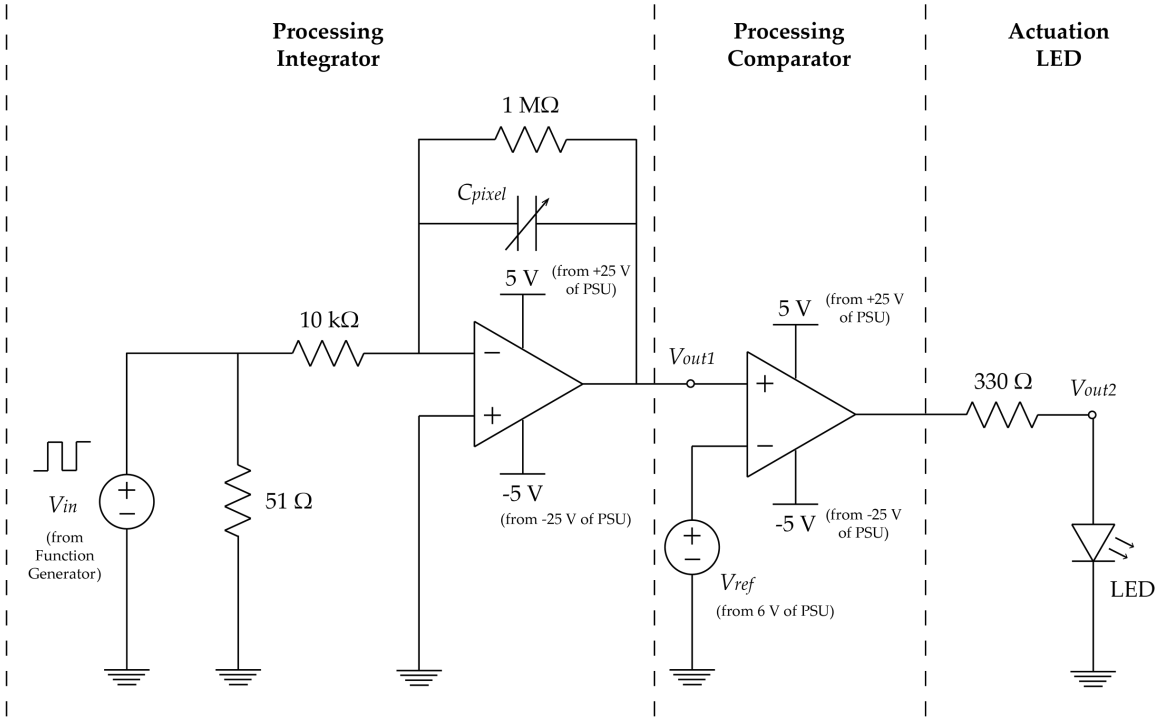

R	Band Colors
51 Ω	Gr Br Bl G
10 kΩ	Br Bl O G
1 MΩ	Br Bl Gr G
330 Ω	O O Br G