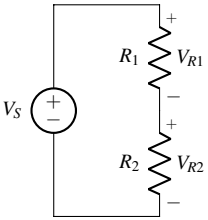
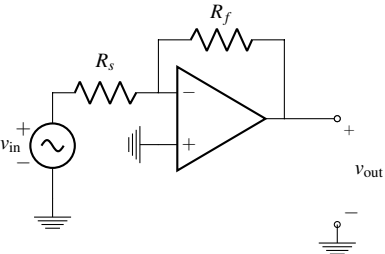
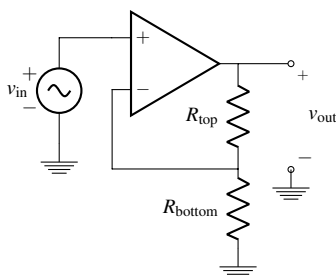
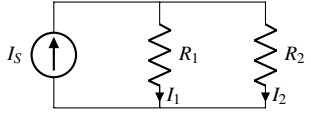
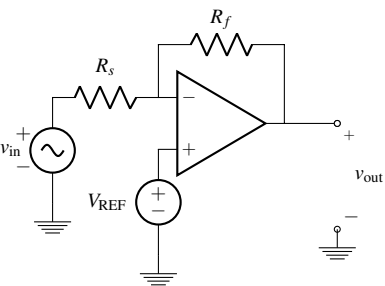
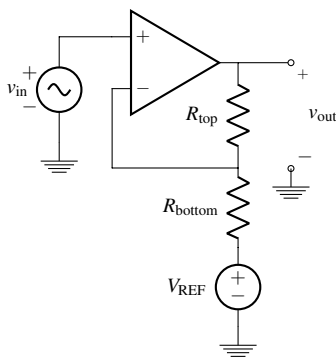
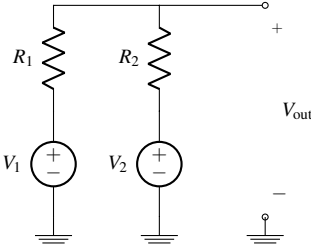
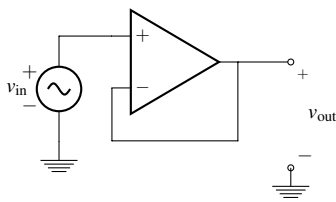


Reference: Op-Amp Example Circuits


<p>Voltage Divider</p>  $V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$	<p>Inverting Amplifier</p>  $v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right)$	<p>Noninverting Amplifier</p>  $v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right)$
<p>Current Divider</p>  $I_1 = I_S \left(\frac{R_2}{R_1 + R_2} \right)$	<p>Inverting Amplifier with Reference</p>  $v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$	<p>Noninverting Amplifier with Reference</p>  $v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$
<p>Voltage Summer</p>  $V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$	<p>Unity Gain Buffer</p>  $v_{out} = v_{in}$	

1. Voltage Summers

Learning Goal: This problem uses basic circuit analysis techniques to find the response of a summer circuit.

Relevant Notes: [Note 19](#) goes different op-amp circuit topology and corresponding derivations.

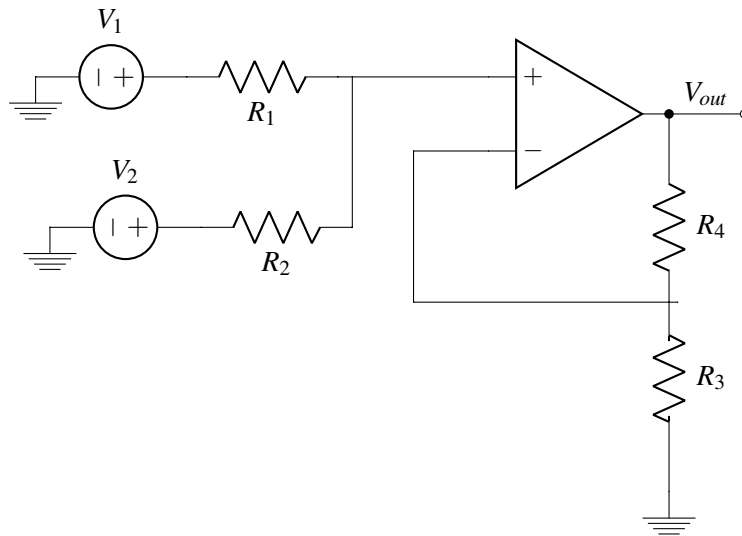- (a) Calculate V_{out} in terms of V_1 and V_2 . Assume that $R_1 = R_2$. Use superposition.



- (b) What values should we select for R_1 , R_2 , R_3 , and R_4 such that $V_{out} = V_1 + 2V_2$?

2. Multi-stage Amplifier

Learning Goal: The objective of this problem is to understand how multiple stages of op-amp circuits can be used to achieve a specific circuit gain.

Relevant Notes: [Note 19 Section 19.5](#) goes over inverting and non-inverting amplifiers.

- (a) What is the range of values that we can scale V_{in} by when using a non-inverting op amp? (What are possible values for the gain?)

- (b) What is the range of values that we can scale V_{in} by when using an inverting op amp? (What are the possible values for the gain?)
- (c) Can you design a single inverting/ non-inverting amplifier with circuit gain $G = 0.5$? If not, what range of gain values is not reachable using a single inverting op amp or a single non-inverting op amp?
- (d) How would you construct a circuit using inverting/ non-inverting amplifiers so that the overall circuit gain is $G = 0.5$?


3. Op Amps as Buffers

Learning Goal: This problem helps understand the operating principle of an op-amp buffer and how it helps with loading.

Relevant Notes: [Note 19 Section 19.7](#) goes different op-amp circuit topology and corresponding derivations.

Now we will revisit a problem that you might have seen before, with our new knowledge of op-amps. We have access to a circuit inside a 'black box' as shown below, with two terminal coming out of it.

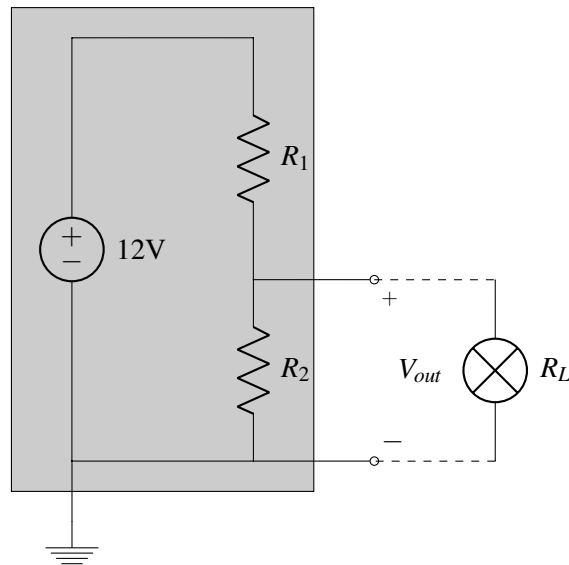- (a) We need a voltage of 6V power a light bulb with resistance R_L . Design R_1 and R_2 inside the black box so that the voltage across R_2 is exactly equal to this required voltage **when the bulb is not connected**; i.e. $V_{R_2} = V_{out} = 6V$.



(b) Now let us connect the bulb R_L across R_2 . What is the voltage across R_1 , R_2 and R_L when the bulb is connected when $R_L = R_2$? Use the values of R_1 and R_2 from the last part. Will the light bulb turn on? What happens if $R_L = 2R_2$?

(c) Using your knowledge of op-amps, how could you resolve this issue of V_{out} changing based on the value of R_L ? Think about how you might use an op-amp buffer.