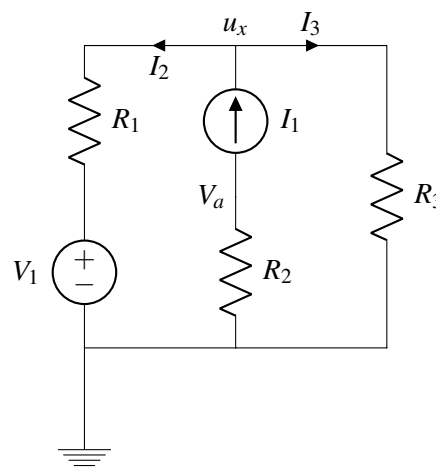


**1. Superposition**

**Learning Goal:** This problem aims to make students familiar with the technique of superposition. It will also show how to nullify different types of sources in the process.


**Relevant Notes:** [Note 15: Section 15.3](#) goes over the principle of superposition.

Solve the following circuit for  $u_x$  using superposition. Let  $R_1 = 10\Omega$ ,  $R_2 = 5\Omega$ ,  $R_3 = 2\Omega$ ,  $V_1 = 12V$ , and  $I_1 = 3A$ .



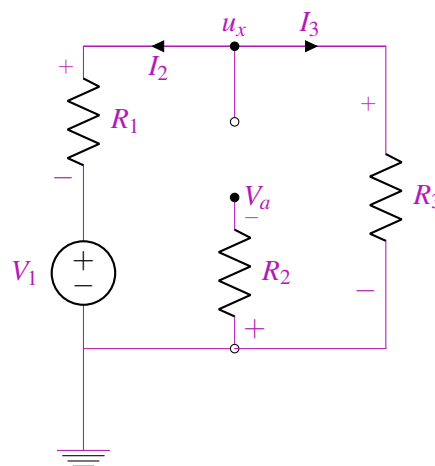(a) Find  $u_x$  when only  $V_1$  is active.

**Answer:** We start off our analysis using superposition by nullifying all independent sources except for one. In this part, we nullify the current source  $I_1$ , replacing it with an open circuit:



Now, all the current flows through  $I_2$  and  $I_3$ , with nothing going through the open circuit or  $R_2$ . Our circuit has been reduced to a single loop, with elements  $V_1$ ,  $R_1$ , and  $R_3$  in series. Notice that this is a voltage divider! Thus, we can write

$$V_{R_3} = V_1 \frac{R_3}{R_1 + R_3}$$


Plugging in our numerical values gives us

$$V_{R_3} = (12\text{V}) \frac{(2\Omega)}{(10\Omega) + (2\Omega)} = 2\text{V}$$

Now  $V_{R_3} = u_x - 0 = u_x$ , so  $u_x = 2\text{V}$

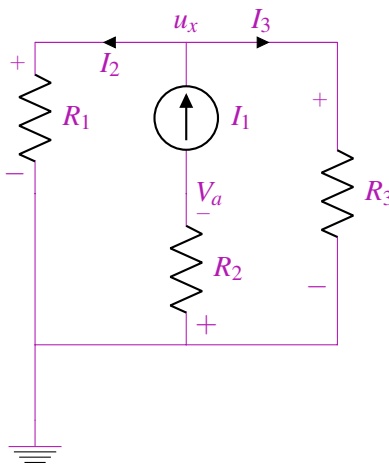(b) Find  $u_x$  when only  $I_1$  is active.

**Answer:** For this part, we continue our analysis using superposition to find  $u_x$  by nullifying the voltage source, which puts a short circuit in its place:



First, we do KCL on the node at  $u_x$ :

$$I_1 = I_2 + I_3$$

Next, we use Ohm's Law on the resistor  $R_1$ . We know one end of the resistor is at voltage  $u_x$  and the other end is connected to ground, so:

$$V = IR$$

$$u_x - 0 = I_2 R_1$$

$$I_2 = \frac{u_x}{R_1}$$

Likewise, we can use Ohm's Law on the resistor  $R_3$ :

$$V = IR$$

$$u_x - 0 = I_3 R_3$$

$$I_3 = \frac{u_x}{R_3}$$

We can substitute both  $I_2$  and  $I_3$  into the KCL equation to solve for  $u_x$ :

$$I_1 = \frac{u_x}{R_1} + \frac{u_x}{R_3}$$

$$I_1 = u_x \left( \frac{1}{R_1} + \frac{1}{R_3} \right)$$

$$u_x = I_1 \frac{R_1 R_3}{R_1 + R_3}$$

Now, we plug in numerical values:

$$u_x = (3\text{A}) \frac{(10\Omega)(2\Omega)}{(10\Omega) + (2\Omega)}$$

$$= 5\text{V}$$

(c) Use your results from the last two parts to find  $u_x$  when all the sources are active.

**Answer:** We have found each individual component using superposition, by zeroing out the current source in part (a) and the voltage source in part (b). Now, to find  $u_x$  when all sources are active, we add together the  $u_x$ 's we found in previous parts. We will also show the algebra here:

$$u_x = u_{x,a} + u_{x,b}$$

$$= V_1 \frac{R_3}{R_1 + R_3} + I_1 \frac{R_1 R_3}{R_1 + R_3}$$

$$= \frac{R_3(V_1 + I_1 R_1)}{R_1 + R_3}$$

From here, we can find  $u_x$  either by plugging in values for  $V_1$ ,  $I_1$ ,  $R_1$ , and  $R_3$ , or taking the answers from part (a) and part (b) and adding them:


$$u_x = 2\text{V} + 5\text{V} = 7\text{V}$$

## 2. Equivalence in Capacitive Networks

**Learning Goal:** This objective of this problem is to practice finding equivalent capacitance for series/parallel network of capacitors.

**Relevant Notes:** [Note 16](#) derives the equivalent capacitance formula for series/ parallel capacitors.

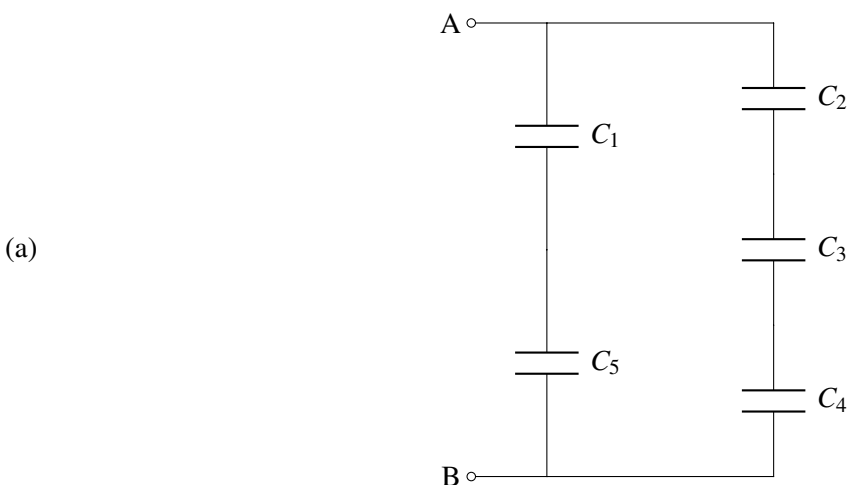
For all of the following networks find an expression or a numerical value for the equivalent capacitance between terminals A and B.



**Answer:** Here we have two branches connected in parallel, one including capacitors  $C_1, C_5$  (which are connected in series) and one including capacitors  $C_2, C_3,$  and  $C_4$  (which are also connected in series). The equivalent capacitance of the left branch is  $C_1||C_5$ , where  $||$  is the parallel operator (i.e.  $a||b = \frac{ab}{a+b}$ ). Similarly, for the right branch, the equivalent capacitance is  $C_2||C_3||C_4$ . Since the two branches are in parallel, we can sum up their equivalent capacitances:

$$C_{AB} = (C_1||C_5) + (C_2||C_3||C_4)$$

(b)

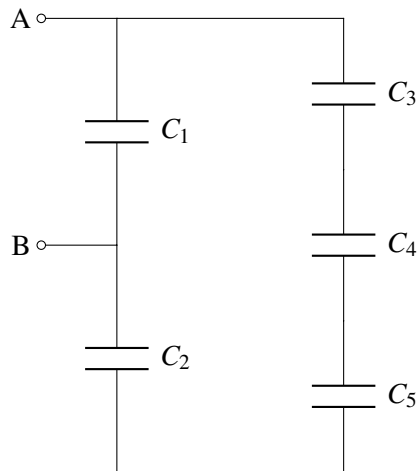

**Answer:**

Here, we have two branches connected in parallel, with the first branch containing only  $C_1$ . The second branch contains  $C_3, C_4, C_5,$  and  $C_2$  in series. The equivalent capacitance of the right branch is  $C_2||C_3||C_4||C_5$ . Then, we can sum this up with  $C_1$  from the left branch to get:


$$C_{AB} = C_1 + (C_2||C_3||C_4||C_5)$$

### 3. Capacitor with a Periodic Current Source


**Learning Goal:** This problem aims to make students familiar with the charging/ discharging response of a capacitor.

**Relevant Notes:** [Note 17](#) covers capacitive behavior in the presence of different types of current sources.

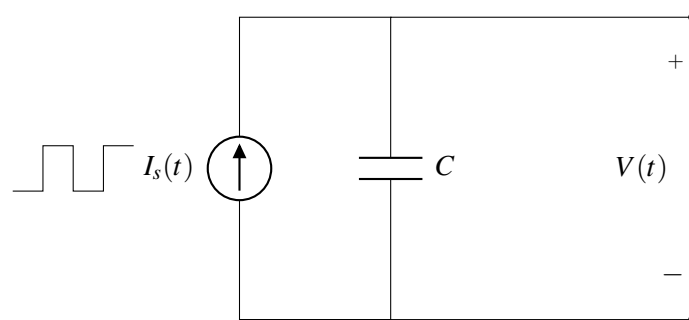Capacitive touchscreen requires detection of capacitance change due to touch. If we connect a known current source  $I_s$  to the capacitor and measure the voltage across the capacitor  $V$ , we will be able to solve for the capacitance  $C$ . So we build the following circuit to measure with a periodic current source:



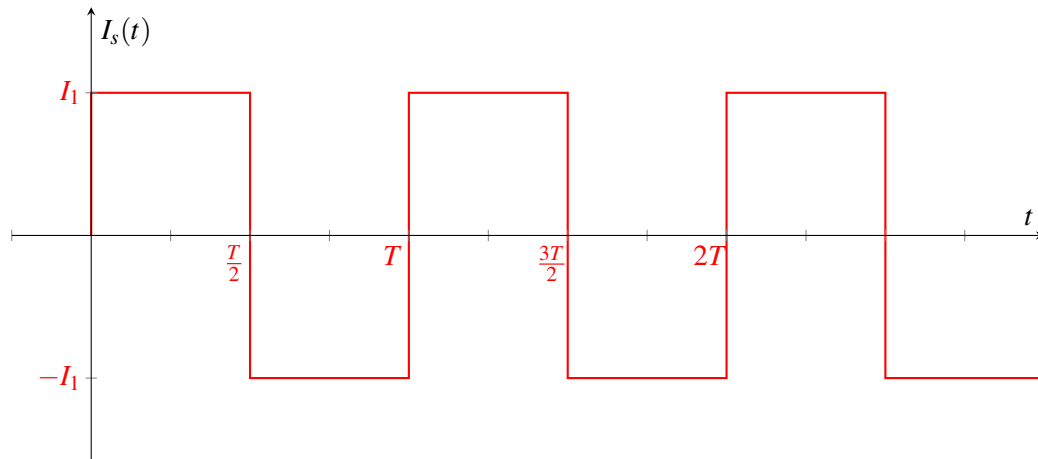(a) Let us assume the current  $I_s$  is a function of time as follows:




What does the voltage  $V$  look like with this current source? Let's assume that the capacitor is initially uncharged (i.e.  $Q = 0$ ). Since  $Q = CV$ , this means that at time  $t = 0$  the voltage  $V = 0$ .

**Answer:** When a constant current source is applied to a capacitor, we know that the voltage obeys the following equation

$$V_C(t) = \frac{I}{C}t + V_C(0). \quad (1)$$

Our periodic current source  $I_s$  is constant from  $t = 0$  to  $t = \frac{T}{2}$ , so we can apply equation ?? over this time period. We know the initial voltage is zero, so:
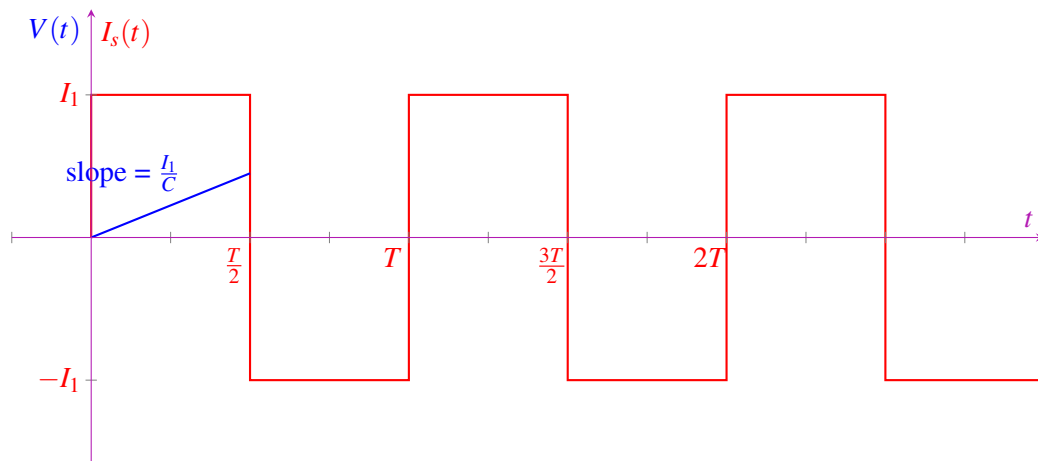
$$V(t) = \frac{I_1}{C}t \quad \text{when } 0 \leq t \leq \frac{T}{2}$$



In order to figure out what happens next, let's consider a more generic version of equation ??:

$$V_C(t) = \frac{I}{C}(t - t_0) + V_C(t_0). \quad (2)$$

With this equation, we can consider an arbitrary starting time  $t_0$  instead of always starting at  $t = 0$ . Plugging in  $t_0 = 0$  yields equation ?. Like equation ?, the above equation is only true when the current is constant.


The next time period with constant current is from  $t = \frac{T}{2}$  to  $t = T$ . Over this time, the current through the capacitor is  $-I_1$ . Since we are starting at time  $\frac{T}{2}$ , we set  $t_0 = \frac{T}{2}$  and plug into equation ??.

$$V(t) = \frac{-I_1}{C} \left( t - \frac{T}{2} \right) + V \left( \frac{T}{2} \right)$$


$$V(t) = \frac{-I_1}{C} \left( t - \frac{T}{2} \right) + \frac{I_1 T}{2C}$$

Combining with our previous relationship yields:

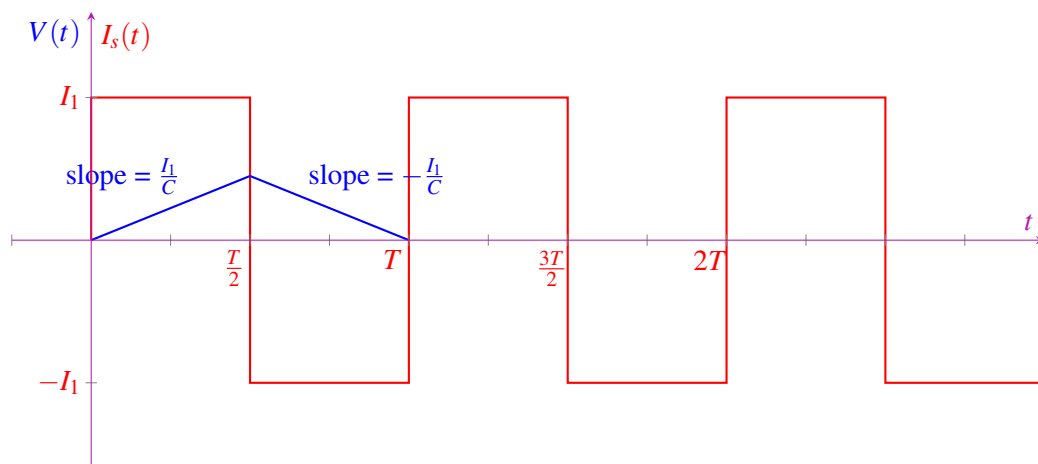
$$V_C(t) = \begin{cases} \frac{I_1}{C} t & \text{when } 0 \leq t \leq \frac{T}{2} \\ \frac{-I_1}{C} \left( t - \frac{T}{2} \right) + \frac{I_1 T}{2C} & \text{when } \frac{T}{2} < t \leq T \end{cases}$$



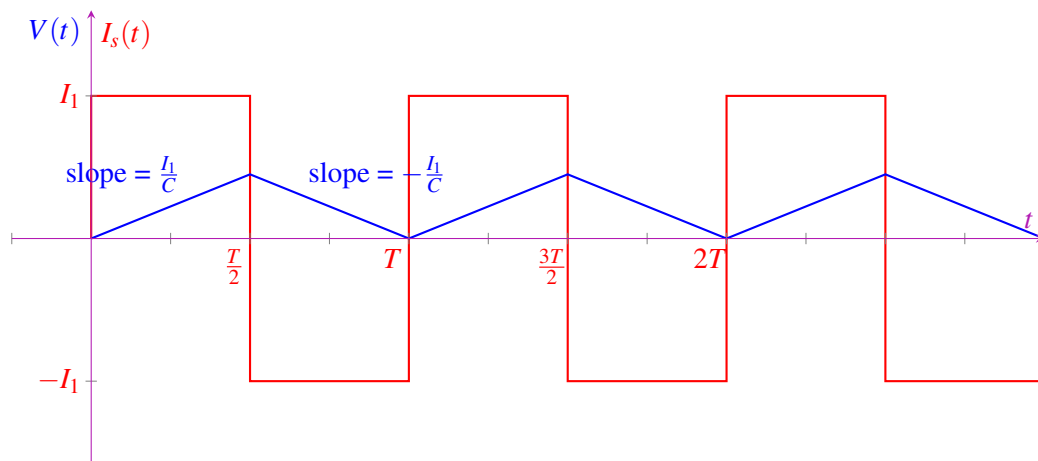To determine the full behavior of  $V(t)$ , we could continue to apply equation ?? for each period of constant current. However, we notice that at  $t = T$ , the voltage and current are the same as they were at  $t = 0$ . Since the current source is periodic (repeats every  $T$ ), the voltage pattern will also repeat.



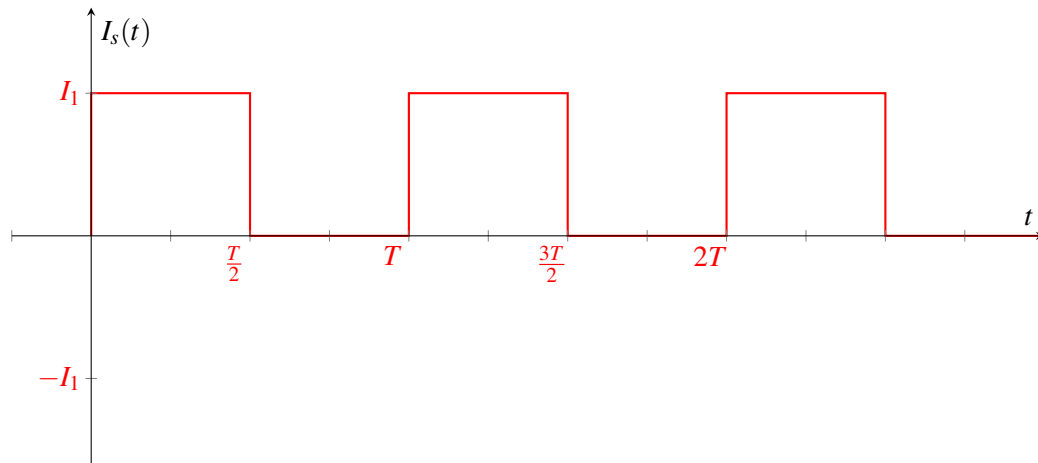(b) Now let us assume the current  $I_s$  is a function of time as follows:



What does the voltage  $V$  qualitatively look like with this current source? Draw out on the above graph how the voltage changes over time, starting at time  $t = 0$ . Let's assume that the capacitor is initially uncharged (i.e.  $Q = 0$ ). Since  $Q = CV$ , this means that at time  $t = 0$  the voltage  $V = 0$ .

**Answer:**

In the first segment, when  $0 \leq t \leq \frac{T}{2}$ , we found in part (a) using equation ?? that

$$V_C(t) = \frac{I}{C}t$$

However, when  $\frac{T}{2} < t \leq T$ ,  $I_s(t)$  is now 0. We again use equation ?? from part (a)

$$V_C(t) = \frac{I}{C}(t - t_0) + V_C(t_0).$$

knowing that  $t_0 = \frac{T}{2}$ . To find  $V_C(t_0)$ , we can use the fact that  $0 \leq t \leq \frac{T}{2}$  when  $t = t_0$  to get  $V_C(t_0) = \frac{I}{C} \frac{T}{2}$ . Plugging these values into equation ?? gives:

$$V_C(t) = \frac{0}{C}(t - \frac{T}{2}) + \frac{I}{C} \frac{T}{2} = \frac{I_1 T}{2C}$$

Qualitatively, this indicates that  $V_C(t)$  is held constant whenever  $I_s(t) = 0$ . However, when  $I_s(t) = I_1$ ,  $V_C(t)$  goes upwards with slope  $\frac{I_1}{C}$ , starting from the constant value of  $V_C(t)$  while its slope is 0.

