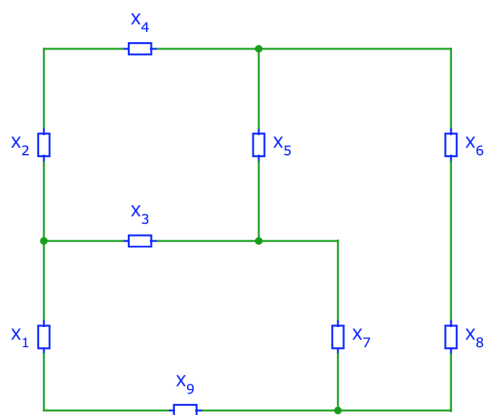


EECS 16A Designing Information Devices and Systems I

Fall 2020 Discussion 6B

1. Nodes and Branches

In the circuit shown below, label and count all nodes and branches.



Answer: There are seven nodes and nine branches.

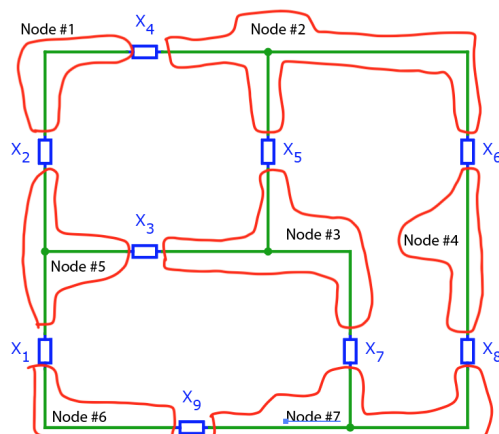


Figure 1: Labeled Nodes


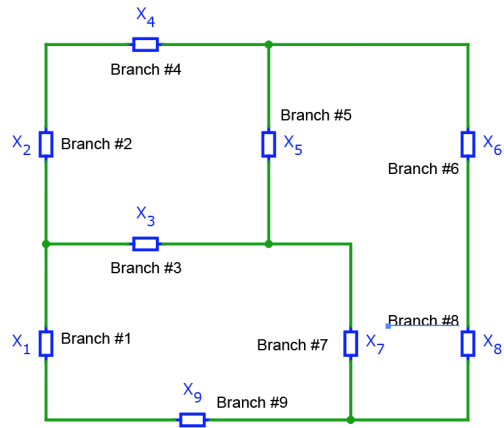


Figure 2: Labeled branches

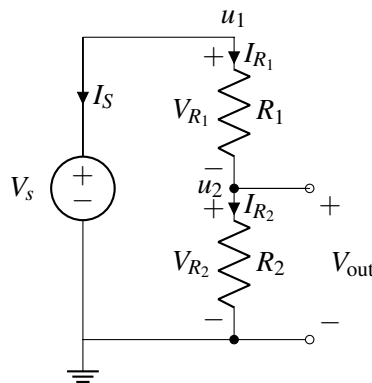2. Voltage Divider

For the circuit below, your goal will be to find the voltage V_{out} in terms of the resistances R_1 , R_2 , and V_s , using NVA (Node Voltage Analysis). The labeling steps (steps 1-4) have already been done for you.




Here is a reminder of the labeling steps followed to get the circuit diagram above:

- **Step 1:** Select a reference (ground) node. Any node can be chosen for this purpose. We will measure all of the voltages in the rest of the circuit relative to this point.
- **Step 2:** Label all nodes with voltage set by voltage sources.
- **Step 3:** Label remaining nodes.
- **Step 4:** Label element voltages and currents, following **Passive Sign Convention** (discussed below).

Passive sign convention

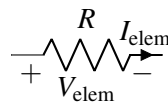
The **passive sign convention** dictates that positive current should *enter* the positive terminal and *exit* the negative terminal of an element. Below is an example for a resistor:




As long as this convention is followed consistently, it does not matter which direction you arbitrarily assigned each element current to; the voltage referencing will work out to determine the correct final sign. When we discuss *power* later in the module, you will see why we call this convention “passive.”

To achieve your goal of *finding* V_{out} , perform the rest of the NVA steps in the boxes below:


Step 5: Write KCL equations for all nodes with unknown voltages.

 A large empty rectangular box intended for the student to write KCL equations for nodes with unknown voltages.


Step 6: Find expressions for all element currents in terms of element voltages and characteristics.

 A large empty rectangular box intended for the student to find expressions for all element currents in terms of element voltages and characteristics.


Step 7: Substitute all element voltages with node voltages found in your step 6 equations.

 A large empty rectangular box intended for the student to substitute all element voltages with node voltages found in their step 6 equations.

 Step 8: Substitute expressions found in step 7 into the KCL equations from step 5.



 
Step 9: Solve for the node voltage values. At this point the analysis procedure is effectively complete - all that's left to do is solve the system of linear equations (by applying Gaussian Elimination, inverting \mathbf{A} , etc.) to find the values for the u 's. Then we can go back to our Step 7 equations and calculate the I 's. Note that in our circuit, $V_{out} = u_2 - 0 = u_2$.




Answer:

Note: The solution will lead you through all of the steps. The result at the end of step 4 will be the circuit in the problem statement above.


Step 1: Select a ground node,

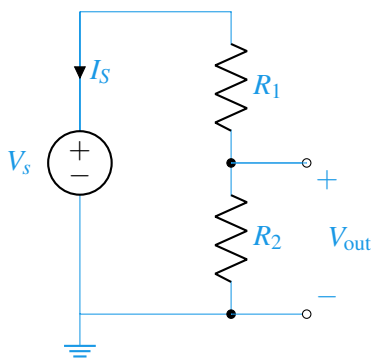

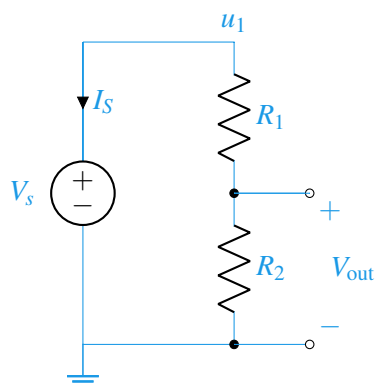
Step 2: Label all nodes with voltage set by voltage sources (denoted below as u_1),



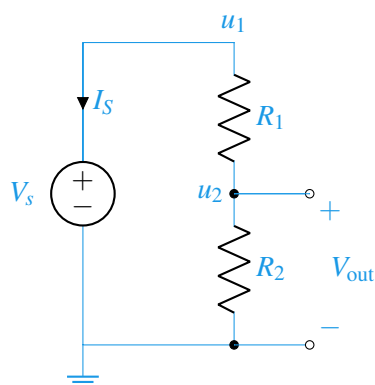Step 3: Label remaining nodes (denoted below as u_2),



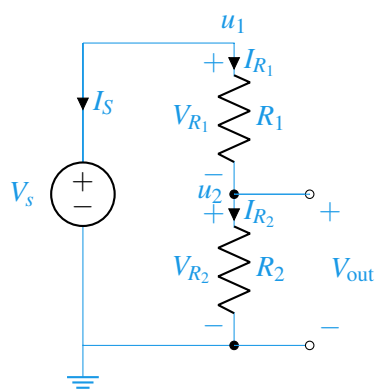Step 4: Label element voltages and currents following passive sign convention,



Step 5: Write KCL equations for all nodes with unknown voltages (namely u_2):

$$I_{R_2} = I_{R_1}$$

Step 6: Find expressions for all element currents in terms of element voltages and characteristics,

$$I_{R_1} = \frac{V_{R_1}}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2}$$

Step 7: Substitute all element voltages with node voltages found in your step 6 equations.

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{u_1 - u_2}{R_1} = \frac{V_s - u_2}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{u_2 - 0}{R_2}$$

Where we used the fact that $u_1 = V_s$

Step 8: Substitute expressions found in 6 into the KCL equations from step 5,

$$I_{R_2} = I_{R_1}$$

$$\Rightarrow \frac{V_s - u_2}{R_1} = \frac{u_2 - 0}{R_2}$$

$$\Rightarrow (V_s - u_2)R_2 = u_2R_1$$

$$\Rightarrow u_2 = \frac{R_2}{R_1 + R_2}V_s$$

Step 9: Since we only have one unknown there is no need to solve a system for equations, we just solve our equation from Step 8 for $u_2 = V_{\text{out}}$ to get:


$$V_{\text{out}} = u_2 = \frac{R_2}{R_1 + R_2}V_s$$

Which is the voltage divider formula derived in lecture.

3. Practice: A Simple Circuit


Use KVL and/or KCL to solve the following circuits.

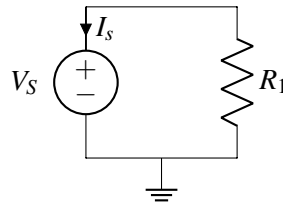- (a) For this problem assume $V_S = 1V$ and $R_1 = 1k\Omega$. Find the current, I_s flowing through the voltage source.



Answer: Notice that in this circuit we only have two nodes, and we know the node voltage of both of them.

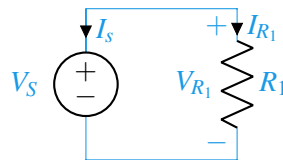Because of that, we can find the current flowing through I_s using KCL and KVL instead of precisely following the algorithm outlined in lecture. Labeling element voltages and currents we have:



Using KVL and Ohm's law we get:


$$V_S = V_{R_1} \quad (\text{KVL}) \quad (1)$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1} = 1mA \quad (\text{Ohm's law}) \quad (2)$$


Finally through KCL on the top node we obtain:

$$I_s + I_{R_1} = 0 \Rightarrow I_s = -I_{R_1} = -\frac{V_S}{R_1} = -1mA \quad (3)$$

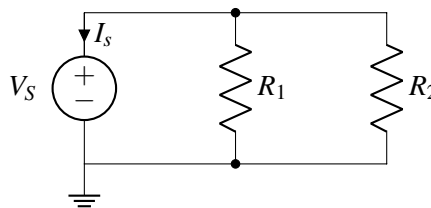- (b) For this problem assume $V_S = 1V$, $R_1 = 2k\Omega$, and $R_2 = 2k\Omega$. Find the current, I_s flowing through the voltage source.



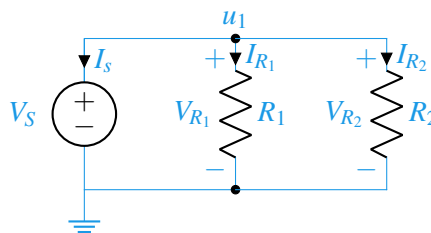Answer: Here we can follow the same procedure since we still have two terminals. Let's label again all element voltages and currents.



Using KVL and Ohm's law:

$$V_S = V_{R_1} = V_{R_2} \quad (\text{KVL}) \quad (4)$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_S}{R_1} \quad (\text{Ohm's law}) \quad (5)$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_S}{R_2} \quad (\text{Ohm's law}) \quad (6)$$

(7)

Then writing out KCL and substituting from above we have:

$$I_{R_1} + I_{R_2} + I_S = 0 \quad (8)$$

$$\frac{V_S}{R_1} + \frac{V_S}{R_2} + I_S = 0 \Rightarrow I_S = - \left(\frac{V_S}{R_1} + \frac{V_S}{R_2} \right) \quad (9)$$

Plugging in,

$$I_S = -1mA \quad (10)$$

Notice that we did not make use of node u_1 or the ground node anywhere.