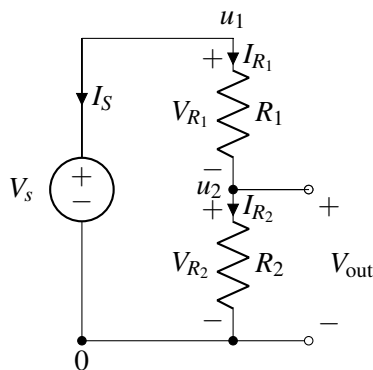


# EECS 16A    Designing Information Devices and Systems I

## Spring 2022    Discussion 6B

### 1. Voltage Divider

For the circuit below, your goal will be to find the voltage  $V_{out}$  in terms of the resistances  $R_1$ ,  $R_2$ , and  $V_s$ , using NVA (Node Voltage Analysis). The labeling steps (steps 1-4) have already been done for you.



Here is a reminder of the labeling steps followed to get the circuit diagram above:

- **Step 1:** Select a reference node and label it 0 (ground). Any node can be chosen for this purpose. We will measure all of the voltages in the rest of the circuit relative to this point.
- **Step 2:** Label all remaining nodes.
- **Step 3:** Label the current through every non-wire element in the circuit.
- **Step 4:** Label element voltages following **Passive Sign Convention**.

Our goal is to *find*  $V_{out}$ . In order to do this, we can use NVA to find equations describing our circuit, and solve the system of linear equations.

**Step 5:** Write KCL equations for all nodes with unknown voltages.


**Step 6:** Write down the IV relationships (Ohm's Law) of each of the non-wire elements.

**Step 7:** Use substitution to solve for  $u_2 = V_{out}$ .


As an additional exercise, write out  $\mathbf{A}\vec{x} = \vec{b}$  where  $\vec{x}$  is a vector of your unknown currents and voltages. Fill in the rows of matrix  $\mathbf{A}$  according to the equations you wrote.

### 2. Passive Sign Convention and Power

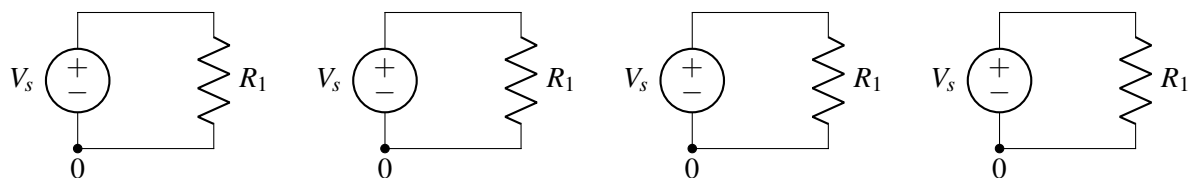
- (a) Below are four copies of a the same single-resistor circuit. On each copy, provide a distinct choice of labels for each circuit's voltage polarities and current directions (there should be 4 possible choices in total!) while keeping with passive sign convention.



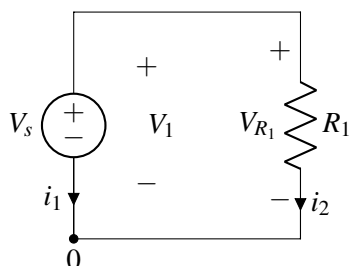- (b) Suppose we consider one of the possible labelings you have found above. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ . Recall that the power dissipated is the rate of electric energy converted into other forms and is given by the equation  $P = IV$ . When the power dissipated by an element is a negative value, it signifies that element is actually supplying electrical power to the circuit.



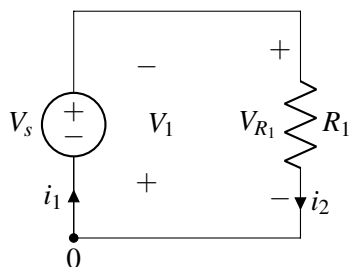- (c) Suppose we choose a second labeling of the circuit as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ .



- (d) Did the values of the element voltages and element currents change with the different labeling? Did the power for each circuit element change? Did the node voltages change? If a quantity didn't change with a difference in labeling, discuss what would have to change for quantity to change.