

---

# EECS 16A    Designing Information Devices and Systems I

## Fall 2020    Discussion 8B


---

### 1. Superposition


For the following circuits:

- Use the superposition theorem to solve for the voltages across the resistors.
- For parts (b) and (c) only, find the power dissipated/generated by all components. Is power conserved?


(a)

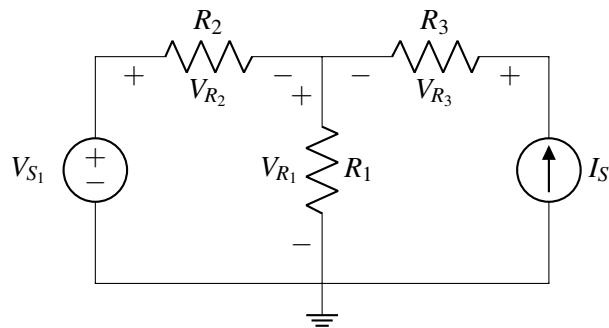

(b)

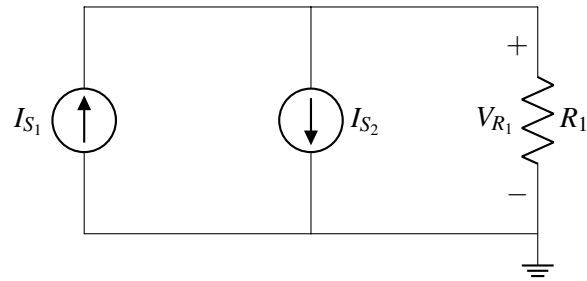


(c)

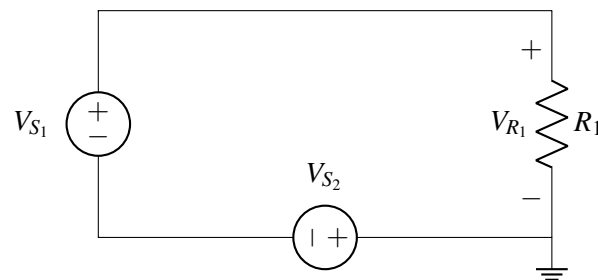
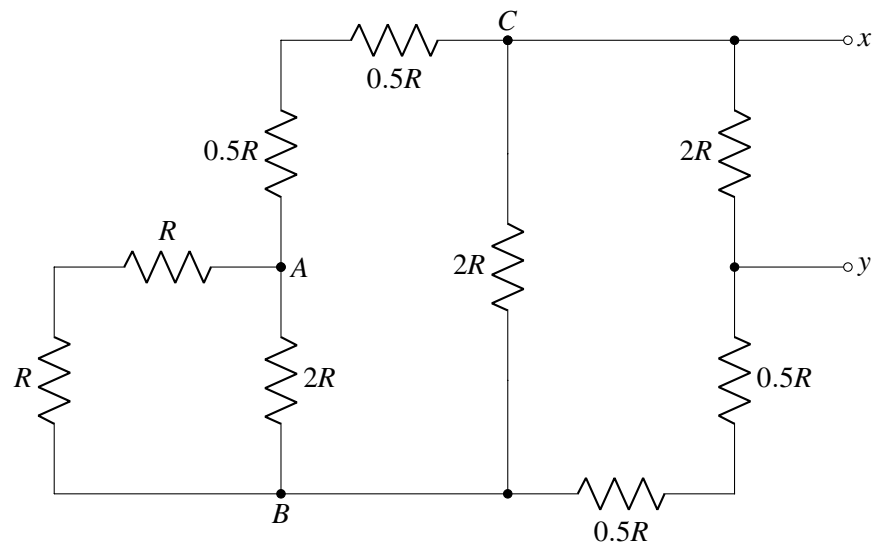
## 2. (Practice) Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals  $x$  and  $y$  using the resistor combination rules for series and parallel resistors.



**3. (Practice) Passive Sign Convention and Power v 2.0**

Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$ ,  $I_s = 0.5\text{ A}$  and  $R_1 = 5\ \Omega$ .

