

---


# EECS 16A     Designing Information Devices and Systems I

## Spring 2023     Exam Prep 12A


---

### 1. Op-amps and Comparators (Spring 2022 Midterm 2 Question 10)

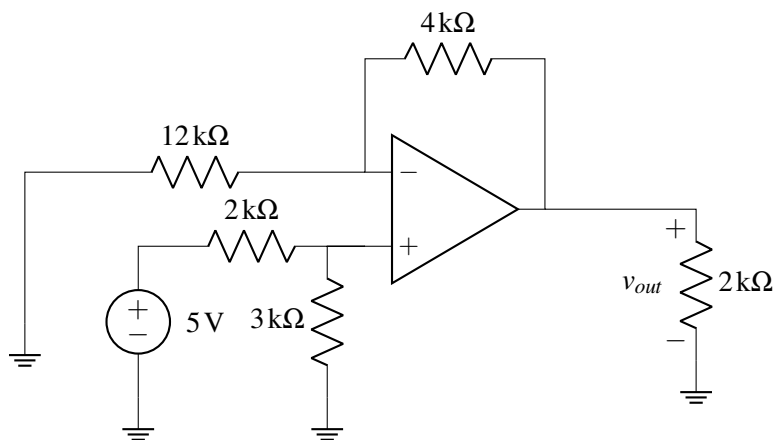(a) You are given the following op-amp in negative feedback. Find  $v_{out}$ .



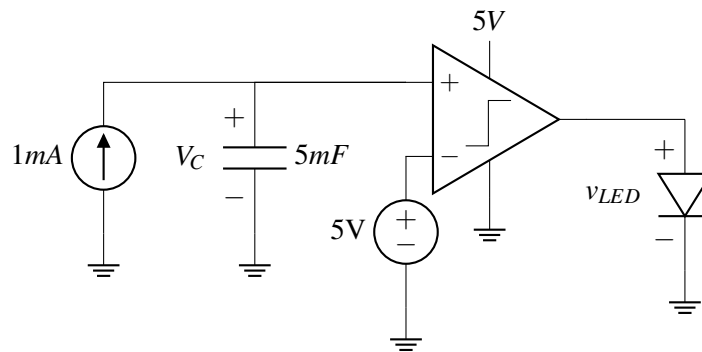
- (b) You are given the circuit below. The capacitor is initially uncharged. At time  $t = 0$ , the current source is turned on. Find  $V_C(t)$ .



- (c) The LED turns on when the voltage across it is greater than 3.3V. Using the same setup as part (b), at what time  $t$  does the LED turn on?

**2. Eigen Circuits (Spring 2022 Midterm 2 Question 11)**

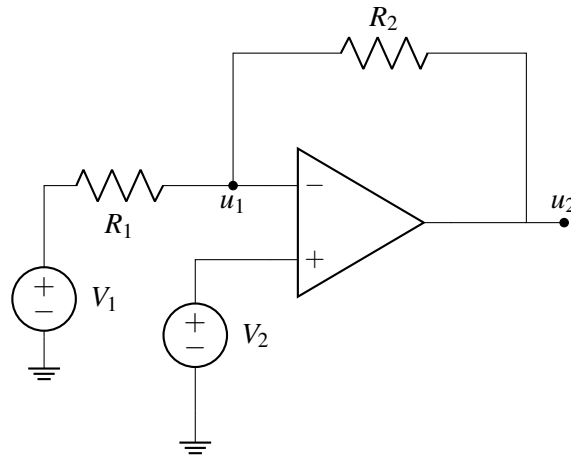- (a) (7 points) You are given the following op-amp circuit in negative feedback.
- i. (5 points) Express  $u_1$  and  $u_2$  in terms of  $V_1$ ,  $V_2$ ,  $R_1$  and  $R_2$ . Assume the op-amp is ideal.



- ii. Write the above equations in the form of  $A\vec{x} = \vec{b}$ .  $\vec{x}$  is  $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$  and  $\vec{b}$  is  $\begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$ .

(b) Assume that after plugging in values for  $R_1$  and  $R_2$ , the matrix  $\mathbf{A}$  you get is  $\begin{bmatrix} 0 & 1 \\ -2 & 3 \end{bmatrix}$ , find the eigenvalue(s) and the eigenvector(s) of this matrix.

(c) Assume you are given another linear circuit with inputs  $V_1$  and  $V_2$  and outputs  $u_1$  and  $u_2$ . The eigenvalues for this circuit are  $\lambda_1 = 1$  and  $\lambda_2 = 2$ . The corresponding eigenvectors are  $\vec{v}_1 = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$ ,  $\vec{v}_2 = \begin{bmatrix} 1 \\ 3 \end{bmatrix}$ . If we want  $u_1 = 3V$ ,  $u_2 = 7V$ , what would the input values be?