
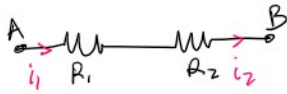


Series Resistors

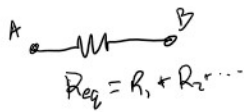


$i_1 = i_2$   
 same current goes through resistors




$R_{eq} = R_1 + R_2 + \dots$

Parallel Resistors

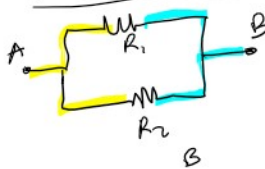

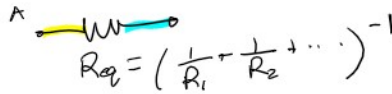
same nodes on either side of the resistors  
 → same voltage




$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$

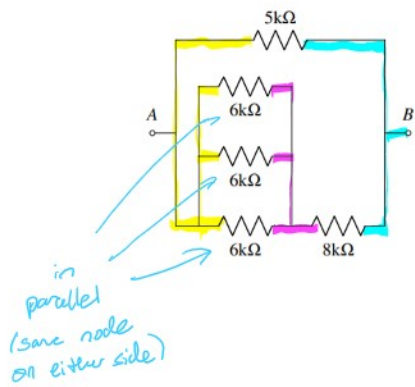**I. Series and Parallel Combinations**

For the resistor network shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.




in parallel (same node on either side)

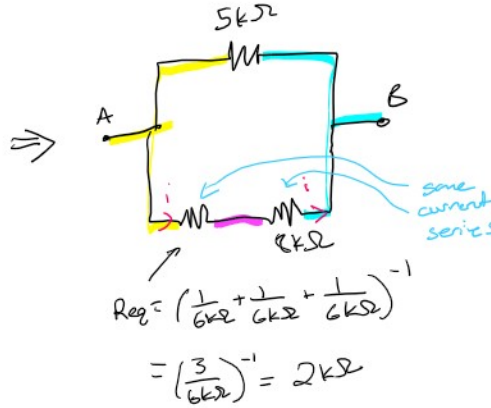


$R_{eq} = \left( \frac{1}{6k\Omega} + \frac{1}{6k\Omega} + \frac{1}{6k\Omega} \right)^{-1}$   
 $= \left( \frac{3}{6k\Omega} \right)^{-1} = 2k\Omega$

same current series

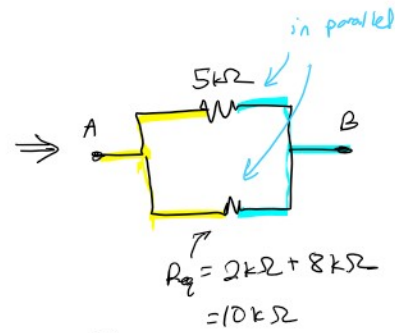


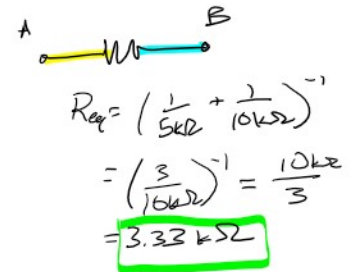$R_{eq} = 2k\Omega + 8k\Omega = 10k\Omega$



$R_{eq} = \left( \frac{1}{5k\Omega} + \frac{1}{10k\Omega} \right)^{-1}$   
 $= \left( \frac{3}{10k\Omega} \right)^{-1} = \frac{10k\Omega}{3}$   
 $= 3.33 k\Omega$

for 2 resistors in parallel

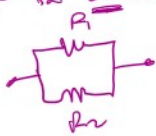

$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$   
 $= \left( \frac{R_1 + R_2}{R_1 R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$

Superposition




\* useful for circuits w/ multiple sources

$V_{out} = V_{out, s_1 \text{ only}} + V_{out, s_2 \text{ only}} + \dots$

↑ desired voltage (could be a current as well)

↑ desired voltage with only one source on

Sources

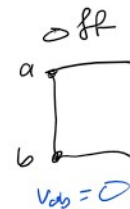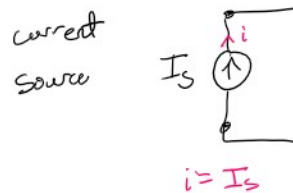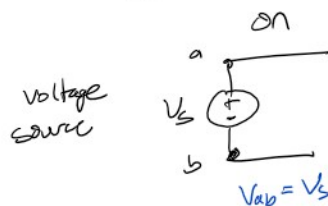


## 2. Superposition

For the following circuits:

- Use the **superposition theorem** to solve for the voltages across the resistors.
- For parts (b) and (c) only, find the power dissipated/generated by all components. Is power conserved?

(a)



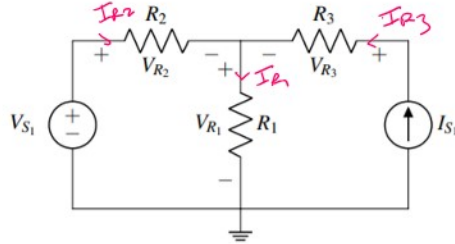


superposition

$$V_{R1} = V_{R1, V_{S1} \text{ only}} + V_{R1, I_{S1} \text{ only}}$$

$$V_{R2} = V_{R2, V_{S1} \text{ only}} + V_{R2, I_{S1} \text{ only}}$$

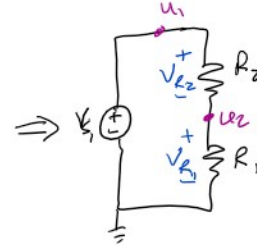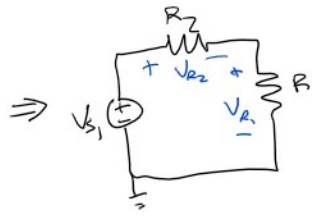
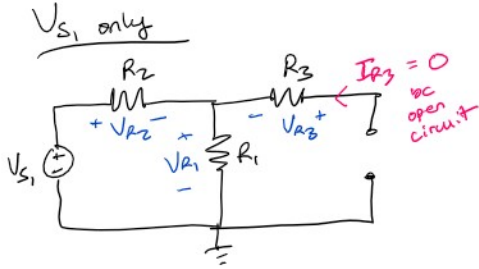
$$V_{R3} = V_{R3, V_{S1} \text{ only}} + V_{R3, I_{S1} \text{ only}}$$



$$V_{R1, V_{S1} \text{ only}} = \frac{R_1}{R_1 + R_2} V_{S1}$$

$$V_{R2, V_{S1} \text{ only}} = u_1 - u_2 = V_{S1} - \frac{R_1}{R_1 + R_2} V_{S1} = \frac{R_2}{R_1 + R_2} V_{S1}$$
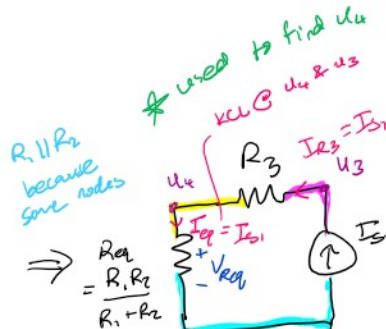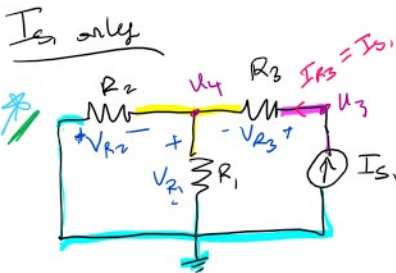
$$V_{R3, V_{S1} \text{ only}} = I_{R3} R_3 = 0$$



$$V_{R3} = u_4 - 0 = I_{eq} R_{eq} = I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$

$$u_4 = I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{R3, I_{S1} \text{ only}} = I_{R3} R_3 = I_{S1} R_3$$

\* from original circuit

$$V_{R1, I_{S1} \text{ only}} = u_4 - 0 = I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$


$$V_{R2, I_{S1} \text{ only}} = 0 - u_4 = -I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{R1} = \frac{R_1}{R_1 + R_2} V_{S1} + I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{R2} = \frac{R_2}{R_1 + R_2} V_{S1} - I_{S1} \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{R3} = I_{S1} R_3$$

(b)

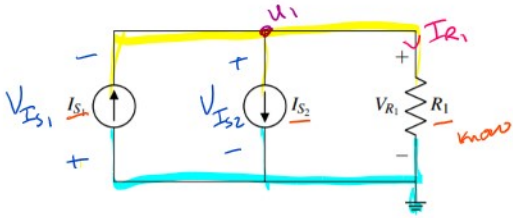

i. KCL @  $u_1$ :  $I_{S1} = I_{S2} + I_{R1}$

$I_{R1} = I_{S1} - I_{S2}$

$V_{R1} = I_{R1} R_1 = (I_{S1} - I_{S2}) R_1 = u_1 - 0$

$V_{I_{S1}} = 0 - u_1 = -V_{R1}$

$V_{I_{S2}} = u_1 - 0 = V_{R1}$

ii.  $P_{R1} = I_{R1} V_{R1} = (I_{S1} - I_{S2})(I_{S1} - I_{S2}) R_1$

$P_{I_{S1}} = I_{S1} V_{I_{S1}} = -I_{S1} (I_{S1} - I_{S2}) R_1$

$P_{I_{S2}} = I_{S2} V_{I_{S2}} = I_{S2} (I_{S1} - I_{S2}) R_1$


is Power conserved?

$P_{R1} + P_{I_{S1}} + P_{I_{S2}} = 0$

plug in to show = 0

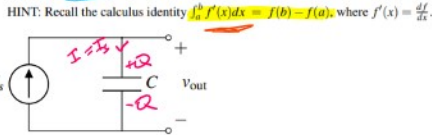3. Current Sources And Capacitors

Given the circuit below, find an expression for  $v_{out}(t)$  in terms of  $I_s$ ,  $C$ ,  $V_0$ , and  $t$ , where  $V_0$  is the initial voltage across the capacitor at  $t = 0$ .



for resistors:  $V = IR$

for capacitors:  $Q = CV$   
 charge on a plate (points to Q), voltage across cap (points to V), capacitance (points to C)

$I = \frac{dQ}{dt}$

$Q = C v_{out}$

$I = \frac{dQ}{dt} = \frac{d}{dt} (C v_{out}) = C \frac{dv_{out}}{dt}$

$\int_0^t \frac{dv_{out}}{dt} dt = \int_0^t \frac{I}{C} dt \Rightarrow v_{out}(t) - v_{out}(0) = \frac{I}{C} (t - 0)$

$v_{out} = V_0 + \frac{I_s t}{C}$

units  
 Coulombs  $Q = CV$   
 $[C] = [F \cdot V]$   
 $[F] = \frac{[C]}{[V]}$   
 $I = \frac{dQ}{dt}$   
 $[A] = \frac{[C]}{[t]}$   
 $\frac{[A]}{[F]} = \frac{[C/t]}{[C/V]} = \frac{[V]}{[t]}$

Then plot the function  $v_{out}(t)$  over time on the graph below for the following conditions detailed below. Use the values  $I_s = 1 \mu A$  and  $C = 2 \mu F$ .

- (a) Capacitor is initially uncharged  $V_0 = 0$  at  $t = 0$ .
- (b) Capacitor has been charged with  $V_0 = +1.5V$  at  $t = 0$ .
- (c) **Practice:** Swap this capacitor for one with half the capacitance  $C = 1 \mu F$ , which is initially uncharged  $V_0 = 0$  at  $t = 0$ .

a)  $v_{out}(t) = 0 + \frac{1 \mu A}{2 \mu F} t = (\frac{1}{2} \frac{V}{ms}) t$

b)  $v_{out}(t) = 1.5V + (\frac{1}{2} \frac{V}{ms}) t$

c)  $v_{out}(t) = 0 + (\frac{1 \mu A}{1 \mu F}) t = (1 \frac{V}{ms}) t$

