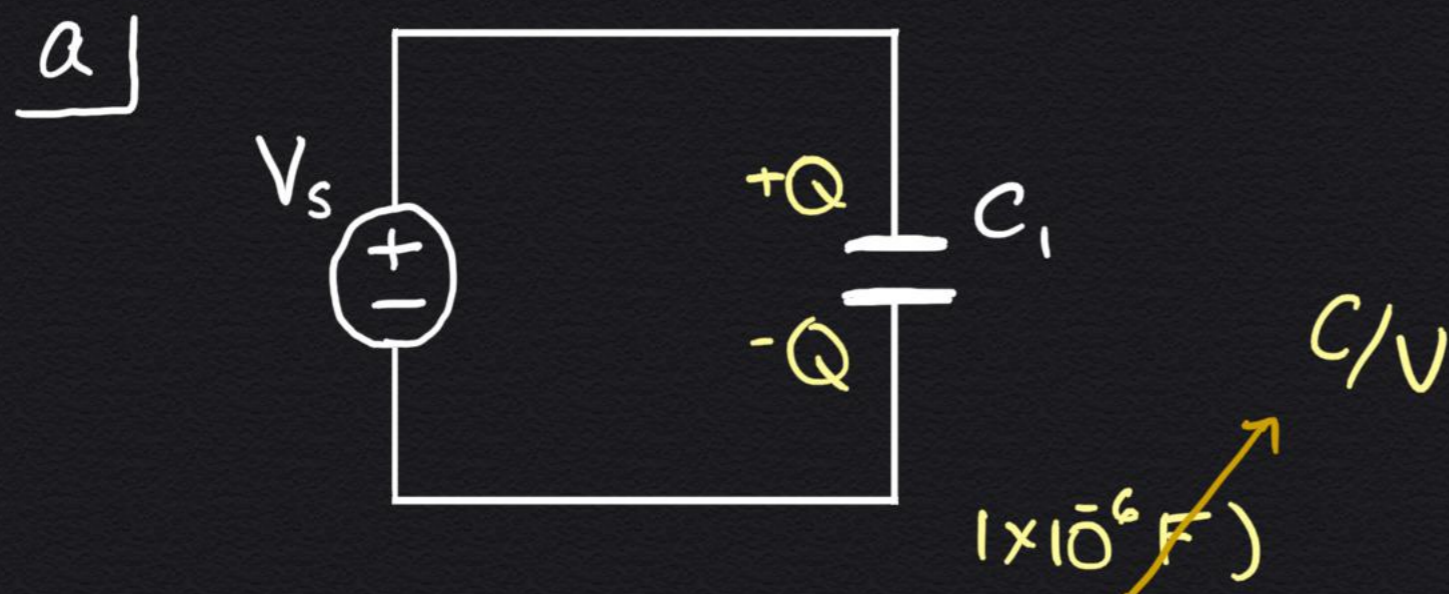


① Given the circuits below, find the voltage across each capacitor and find the charge and energy on each as well:

$$C_1 = 1\mu\text{F} \quad C_2 = 3\mu\text{F} \quad V_s = 1\text{V}$$



Recall:

$$* C = \frac{Q}{V}$$

$$* E = \frac{1}{2} CV^2$$

$$* \text{Metric: } m \sim 10^{-3} \\ \mu \sim 10^{-6} \\ n \sim 10^{-9}$$

\* Units:

$$\hookrightarrow \text{Farad} = \frac{\text{Coulomb}}{\text{Voltage}}$$

$$\hookrightarrow \text{Joule} = \text{Coulomb} \times \text{Voltage}$$

$$* C_{\text{EQ}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$* Q = C_1 V_s = (1\mu\text{F})(1\text{V})$$

$$= 1 \times 10^{-6} \frac{\text{C}}{\cancel{\text{V}}} \text{V}$$



$$= 1\mu\text{C}$$

$$\frac{1\mu\text{C}}{1\text{V}}$$

$$* E = \frac{1}{2} CV^2 = \frac{1}{2} (1\mu\text{F})(1\text{V})^2$$

$$= \frac{1}{2} 1\mu\text{C} \frac{1\text{V}^2}{1\text{V}} = \frac{1}{2} \mu\text{C} \cdot \text{V} = \frac{1}{2} \mu\text{J}$$

$$= 500 \text{ nJ}$$

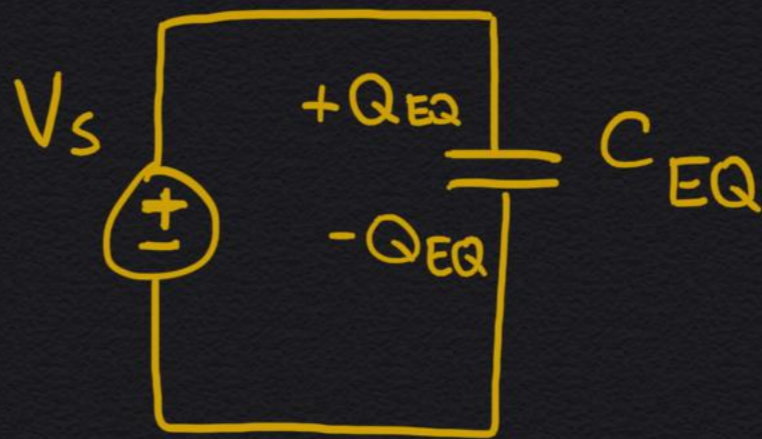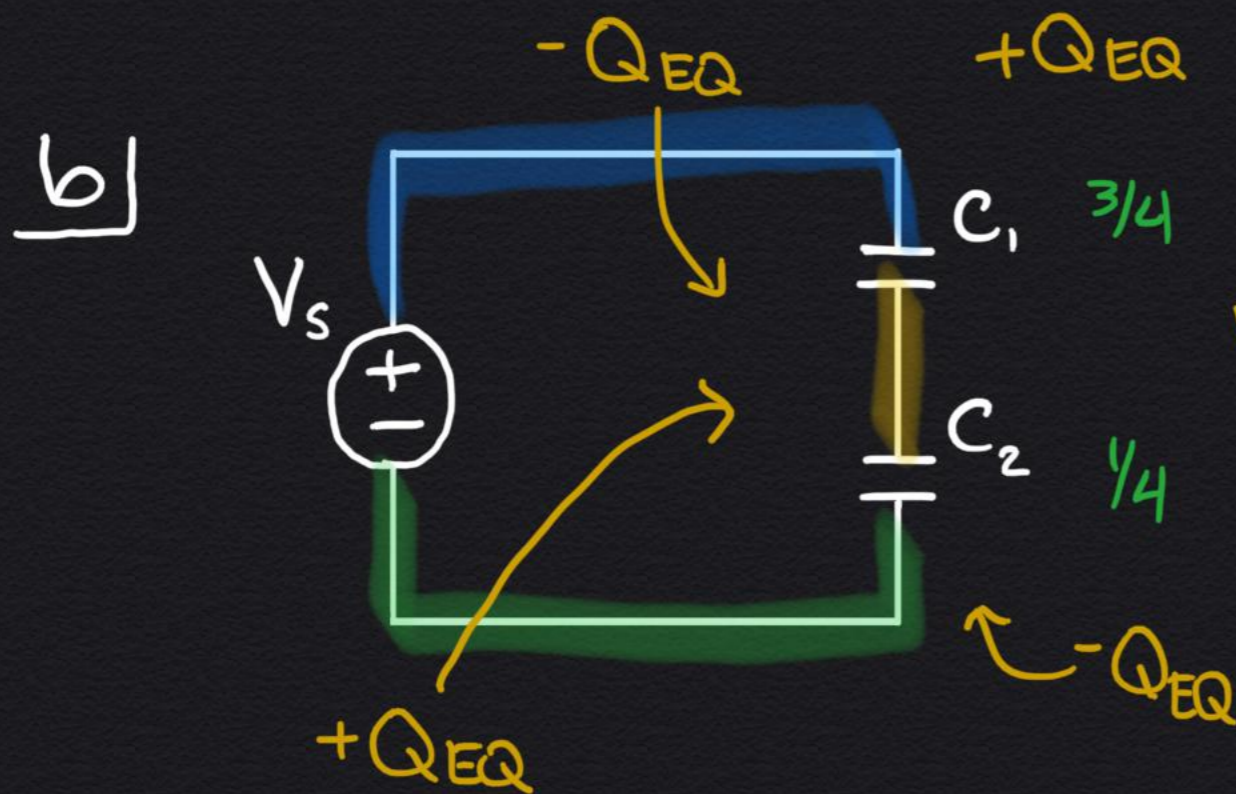

- $C_{EQ} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(1 \mu F)(3 \mu F)}{(4 \mu F)} = \frac{3}{4} \mu F$

- $Q_{EQ} = C_{EQ} V_s = \left(\frac{3}{4} \mu F\right) (1 V) = \left(\frac{3}{4} \frac{\mu C}{V}\right)$

$$V_1 = \frac{Q_{EQ}}{C_1} = \frac{3/4 \mu C}{1 \mu F} = \frac{3}{4} V = \frac{3}{4} \mu C$$

$$V_2 = \frac{Q_{EQ}}{C_2} = \frac{3/4 \mu C}{3 \mu F} = \frac{1}{4} V$$


$$E_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (1 \mu F) \left(\frac{3}{4} V\right)^2 = \frac{9}{32} \mu C \cdot V = \frac{9}{32} \mu J$$

$$E_2 = \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (3 \mu F) \left(\frac{1}{4} V\right)^2 = \frac{3}{32} \mu C \cdot V = \frac{3}{32} \mu J$$

2

Find  $V_{out}(t)$  in terms of  $I$ ,  $C$ ,  $V_0$ , and  $t$ .

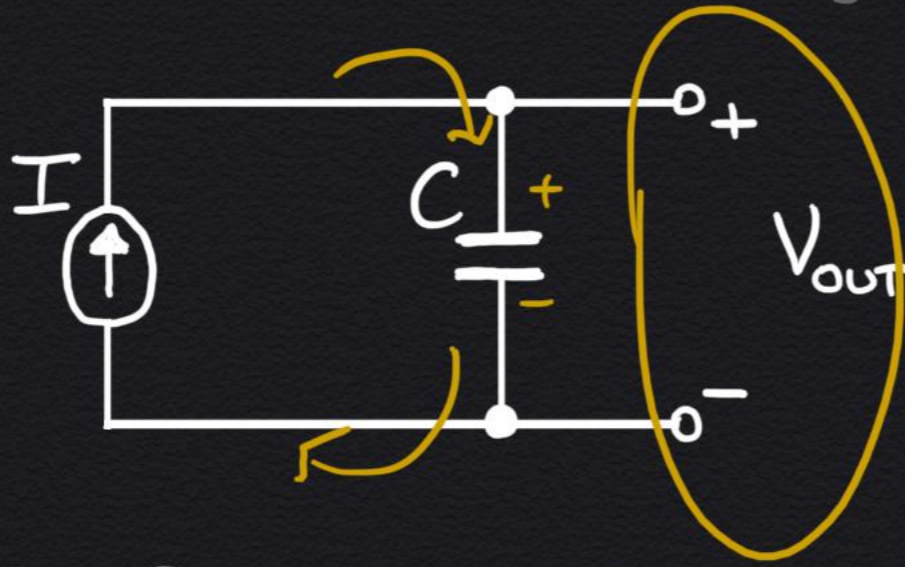(Note:  $V_0$  is the initial voltage  $V_{out}(0)$ )



$$I = 1 \text{ mA}$$

$$C = 2 \mu\text{F}$$

Hint:

$$I = \frac{dQ}{dt} \leftrightarrow V = \frac{Q}{C}$$

Plot this function for the following conditions:

a)  $V_0 = 0 \text{ V}$

b)  $V_0 = 1.5 \text{ V}$

c)  $V_0 = 0 \text{ V}$   $C = 1 \mu\text{F}$

$$V = \frac{Q}{C} \rightarrow \frac{dV}{dt} = \left(\frac{1}{C}\right) \cdot \frac{dQ}{dt} = \left[\frac{I}{C}\right]$$

$$\left\{ V(t) = V_0 + \left(\frac{I}{C}\right)t \right\}$$

$$\int_0^t \left( \frac{dV}{dt'} \right) dt' = V(t) - V(0)$$

$$= \int_0^t \frac{I}{C} dt' = \frac{I}{C} \int_0^t 1 dt'$$


$$V(t) = V_0 + \left( \frac{I}{C} \right) t$$

$\frac{mC}{s} = \frac{\mu C}{mS}$

\*  $y = mx + d$

$$m_{a,b} = \frac{I}{C} = \frac{1 \text{ mA}}{(2 \mu\text{F})} = \frac{1}{2} \cdot \frac{V}{mS}$$
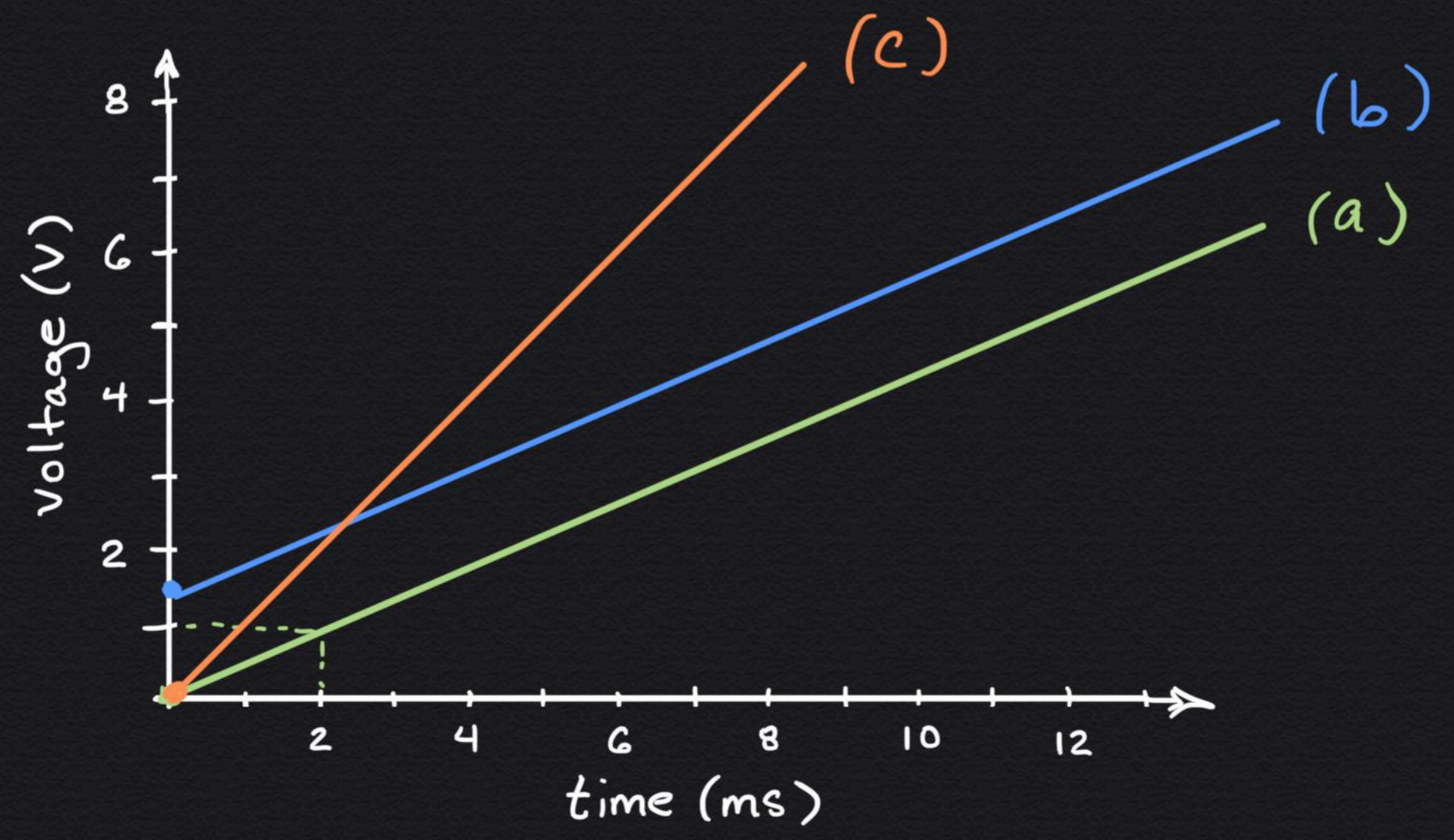
$$m_c = \frac{1 \text{ mA}}{1 \mu\text{F}} = 1 \frac{V}{mS}$$



(Bonus content! Not part of the testable curriculum)


Physics Time:



$$E = k \frac{q_1 q_2}{r} = q_1 \left( k \frac{q_2}{r} \right)$$

Suppose we start "assembling charges"

(4)

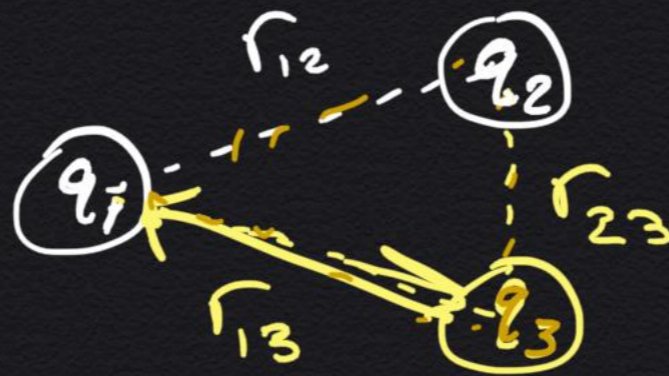

(N)

Energy of 3 charges:  $E = k \left( \frac{q_1 q_2}{r_{12}} + \frac{q_1 q_3}{r_{13}} + \frac{q_2 q_3}{r_{23}} \right)$

Energy of 'N' Charges:

$$= k \sum_i^N q_i \sum_{\substack{j > i \\ j \neq i}}^N \frac{q_j}{r_{ij}}$$

$$= k \sum_i^N q_i \frac{1}{2} \sum_{\substack{j \neq i \\ j \neq i}}^N \frac{q_j}{r_{ij}}$$

$$= \frac{1}{2} \sum_i^N q_i \left( k \sum_{\substack{j \neq i \\ j \neq i}}^N \frac{q_j}{r_{ij}} \right)$$

$V_i$

Recall...  $C = \frac{Q}{V}$

$$E = \frac{1}{2} \sum_i^N q_i V_i$$

$$E = \frac{1}{2} C V^2$$
$$\equiv \frac{1}{2} Q V$$

