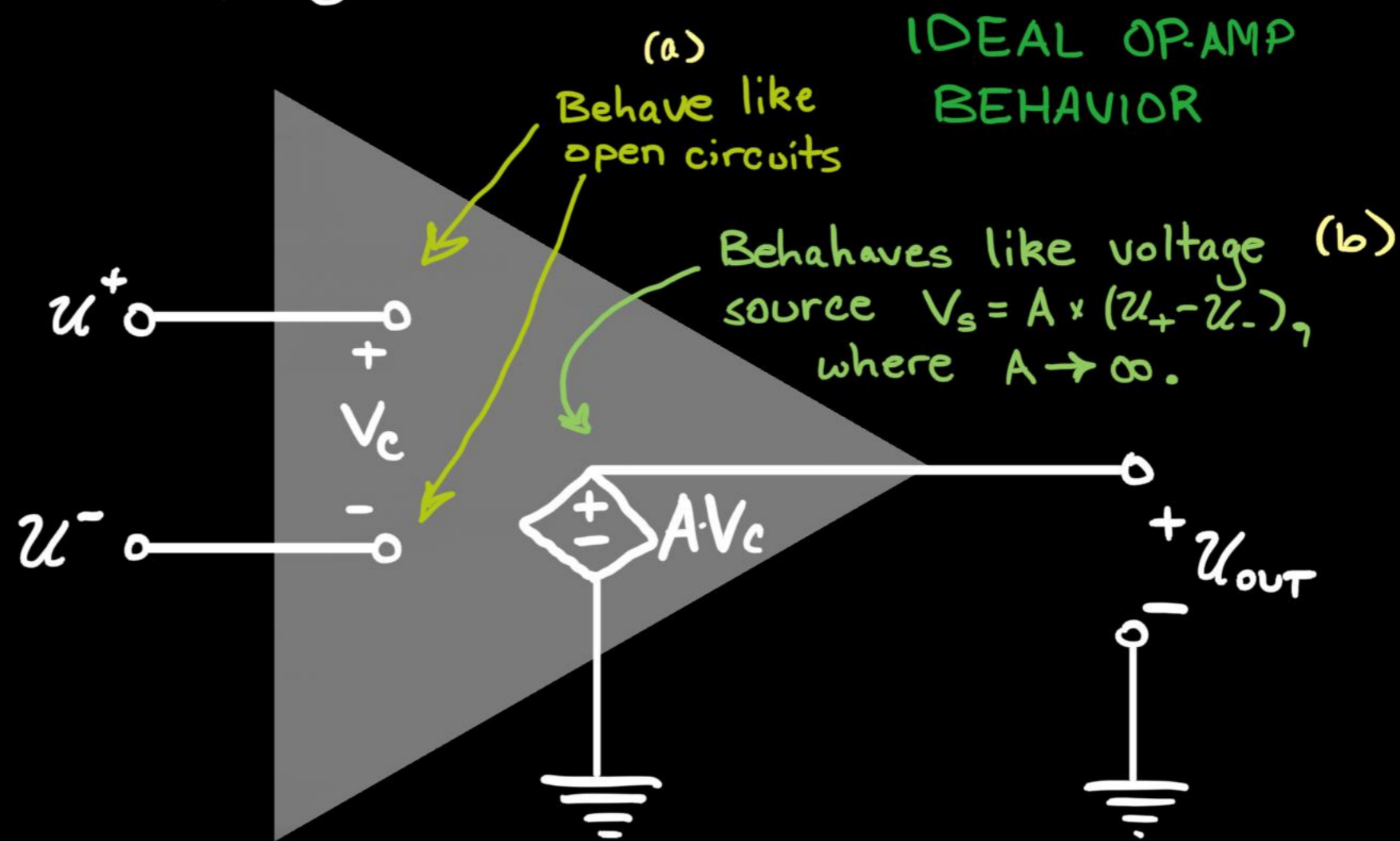


① Op-amp rules:

Equivalent
Circuit
Model:



a) What are the currents flowing into the u^\pm terminals?


$$I_{u_+} = I_{u_-} = 0$$

b) If we connect a resistor R_L across u_{out} , does u_{out} change?

No! u_{out} is independent of R_L , since our op-amp model output is a voltage source.

c/d) Consider the circuit:

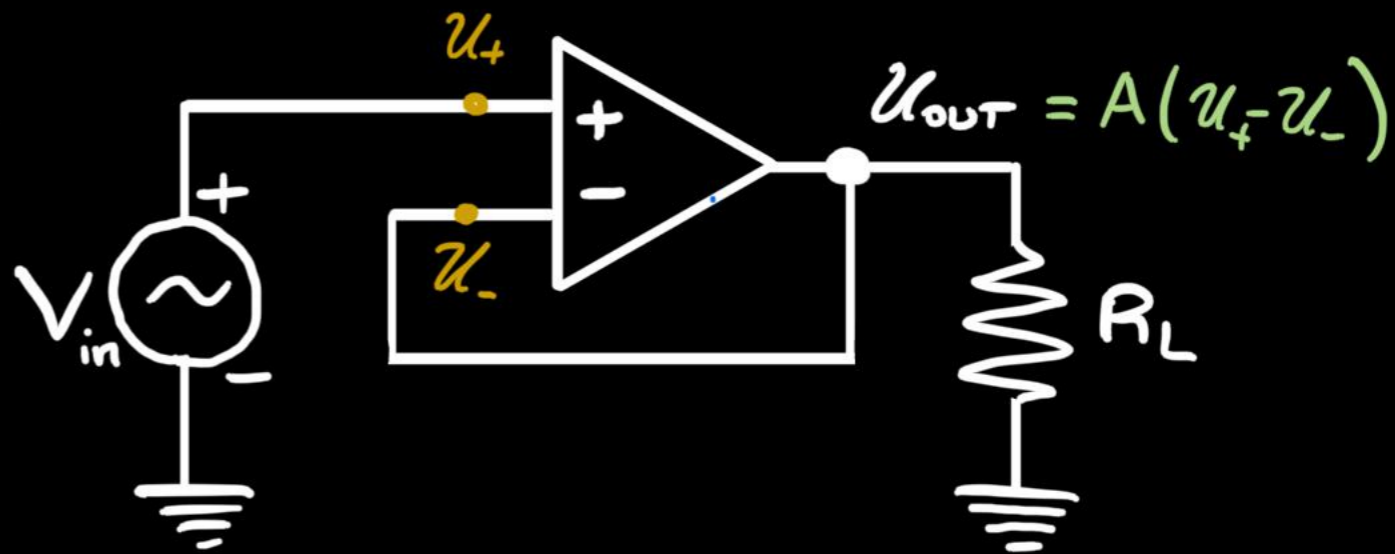- What is U_{OUT} for an ideal op-amp ($A \rightarrow \infty$)?
- Consider finite A and find U_{OUT} :



Same Node \swarrow
 $V_{in} = U_+ = U_- = U_{OUT}$
 Same Node \searrow

" $A \rightarrow \infty$ ideal negative-feedback condition:"

∞
 $A(U_+ - U_-) = U_{OUT}$
 $= 0$

$U_{OUT} = V_{in}$


$U_{OUT} = A(U_+ - U_-)$
 $U_{OUT}(1 + A) = A V_{in}$

$U_{OUT} = \left(\frac{A}{A+1}\right) V_{in}$

$U_{OUT} = \left(\frac{1}{1+(1/A)}\right) V_{in}$

② Comparators

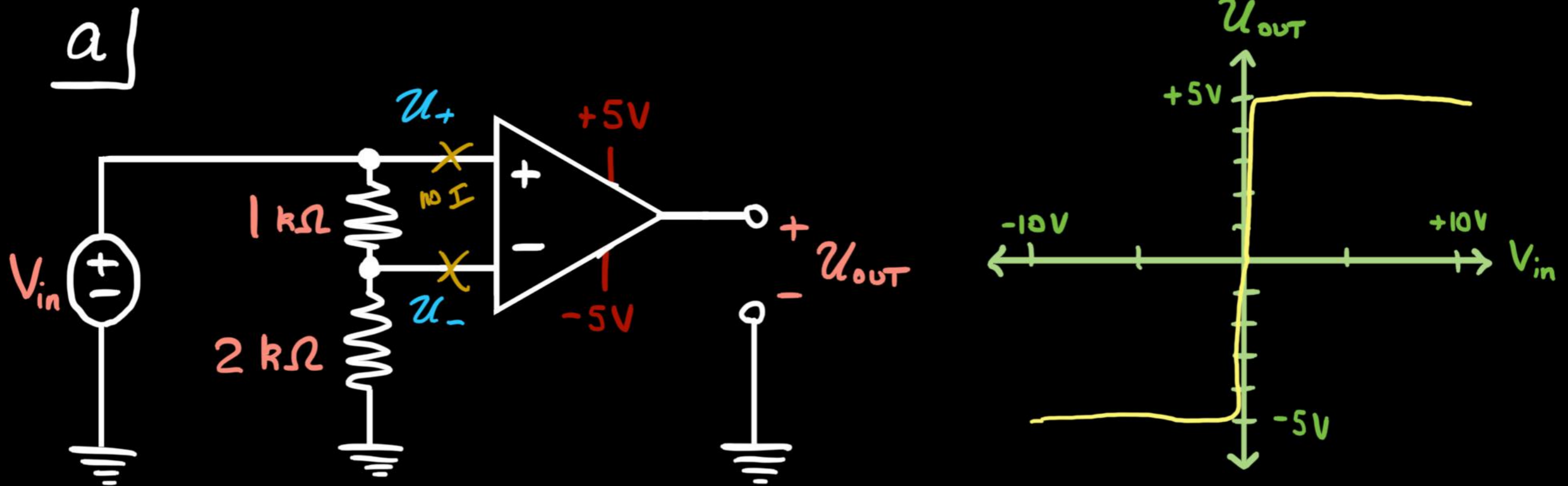For the following circuits, plot $u_{out}(V_{in})$ on the domain $V_{in} \in [-10, +10]V$: $A \sim 10^6$





$$u_+ = V_{in}$$

$$u_- = V_{in} \left(\frac{R_2}{R_1 + R_2} \right) = \frac{2}{3} V_{in}$$

$$u_{out} = A(u_+ - u_-) = A \left(V_{in} - \frac{2}{3} V_{in} \right) = A \underline{\underline{V_{in}}} \cdot \frac{1}{3}$$

b)

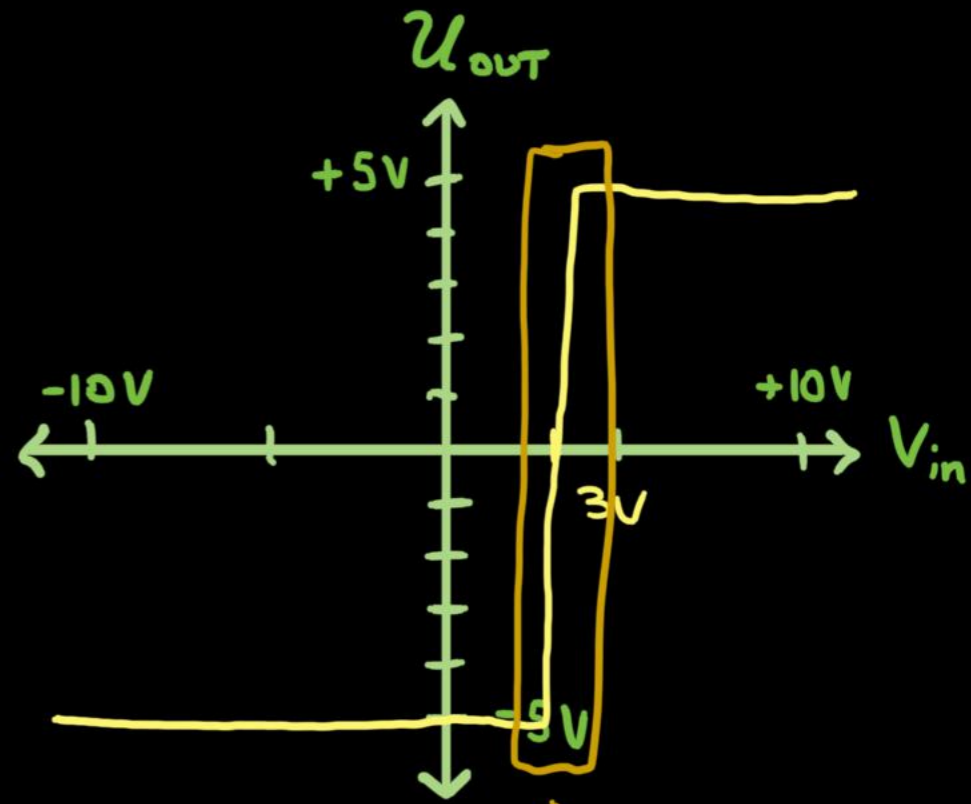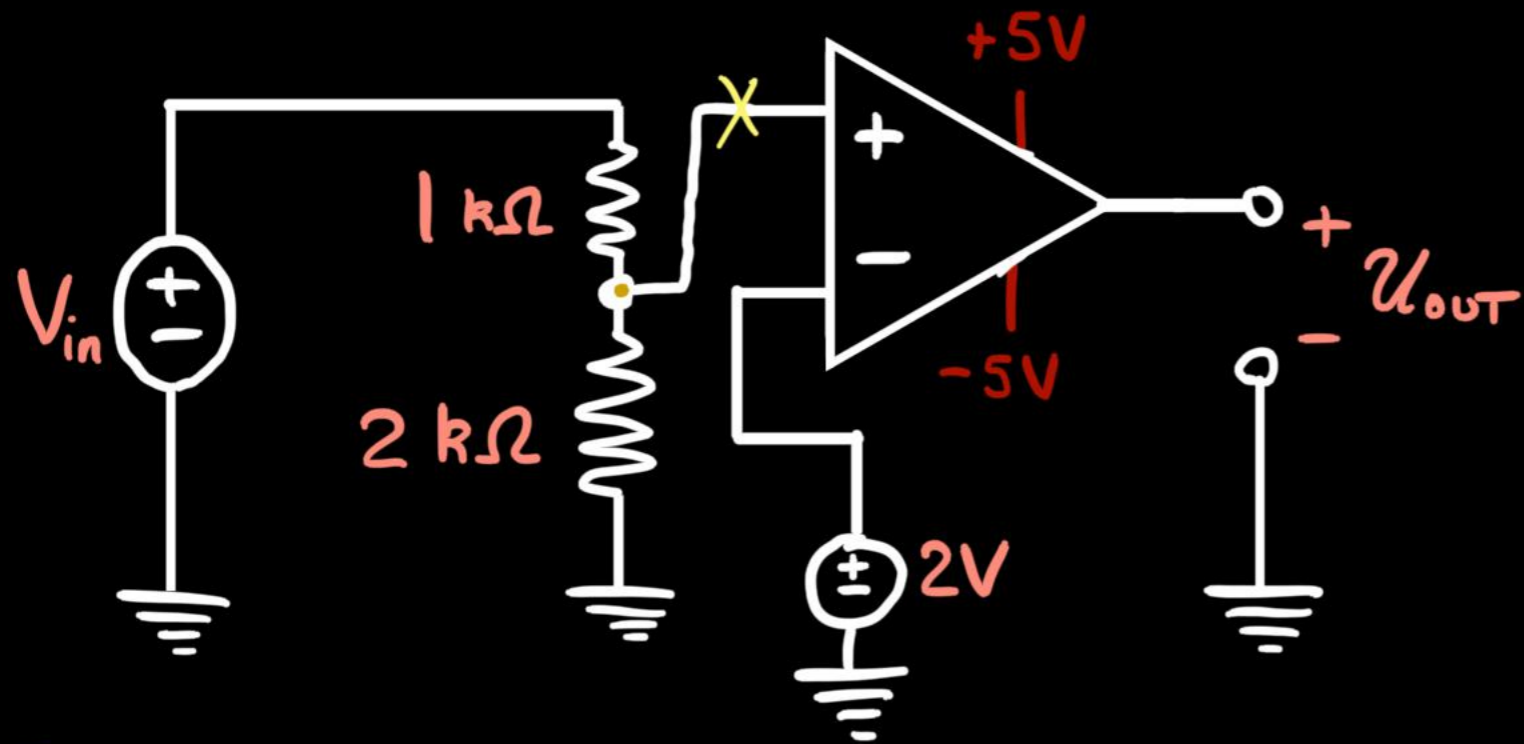

$$\begin{aligned}
 U_+ &= V_{in} \left(\frac{2}{3} \right) \\
 U_- &= 2
 \end{aligned}
 \Rightarrow U_{OUT} = A \cdot \left(\frac{2}{3} V_{in} - 2 \right)$$

$$= \frac{2}{3} A (V_{in} - 3)$$

