

---

# EECS 16A    Designing Information Devices and Systems I

## Fall 2020    Homework 8

---

**This homework is due October 23, 2020 at 23:59.**

**Self-grades are due October 26, 2020, at 23:59.**

### Submission Format

Your homework submission should consist of **one** file.

- `hw8.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

Submit the file to the appropriate assignment on Gradescope.

### 1. Reading Assignment

For this homework, please read Note 15: Section 15.3 to learn about superposition, a concept that can help to simplify circuit analysis. Also read Note 15: Sections 15.7-15.8, which will explain the idea of finding the equivalent resistance. Please also reread Note 14 to review the idea of 2D touchscreen. You are always encouraged to read beyond this as well.

- As a part of superposition, you need to zero out independent sources. What circuit elements are equivalent to a zeroed voltage source and zeroed current source, respectively?
- If you connect three resistors (each with value  $R$ ) in series, what will be the equivalent resistance? What happens if you connect these resistors in parallel?


### 2. Maximum Power Transfer

*(Contributors: Craig Schindler, Gireeja Ranade, Panos Zarkos, Urmita Sikder, Sashank Krishnamurthy)*

**Learning Goal:** *This problem shows how the power dissipated in the load depends on the value of the load resistance. It also helps to understand the condition required for maximum power transfer.*

Smartphones use "bars" to indicate strength of the cellular signal. Fewer "bars" translate to slow or no connectivity. But what do these "bars" actually stand for? Voltage, current? Well, not quite. Good radio (a cellular modem is a particular type of radio) reception depends on the **power received at the receiver**. Communication theory tells us that higher received signal power enables higher data rates. To that end, we design a receiver that maximizes the power received, and hence connection speed.

A typical receiver consists of an antenna and receiver circuits. The antenna receives the radio waves propagating in space, and converts it into electrical voltages and currents. A very good abstraction used by circuit designers is to **model the antenna as a voltage source  $V_S$ , with a series resistance  $R_S$** . The typical values of  $V_S$  in a real cellular receiver are in the range of micro- or milli-volts ( $10^{-6}$  and  $10^{-3}$ , respectively) and the typical values of resistance  $R_S$  are usually  $50\Omega$  or  $75\Omega$ , depending on how the antenna is designed. The receiver circuits are quite complex and will be covered in detail in EE142 "Integrated Circuits for Communications". However, a standard abstraction is to **model these receiver circuits as a load resistance  $R_L$**  to the antenna, as shown in the figure below.

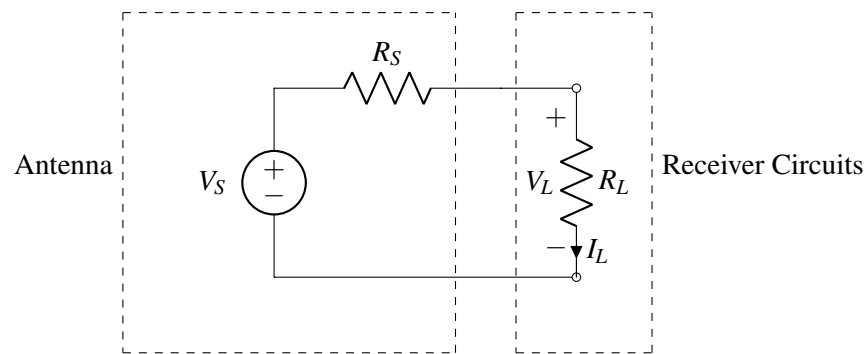

Models are very important in engineering design for their ability to abstract away details when they are not needed and are the key to successful design of complex systems. We will discuss the use and properties of electronic circuit models further in class.

Use the following component values for your calculations:  $V_S = 100\mu\text{V}$ , and  $R_S = 50\Omega$ .

- (a) Consider any value of  $R_L$  within the range:  $0 \leq R_L \leq \infty$ . Find the value of  $R_L$  that maximizes the **voltage**  $V_L$  across resistor  $R_L$ . Calculate the values of  $V_L$ ,  $I_L$ , and the power  $P_L$  dissipated by resistor  $R_L$  for the value you found.

(Hint: The antenna voltage  $V_S$  and the resistance  $R_S$  are fixed. However, you are free to choose the value of  $R_L$  in order to maximize the voltage  $V_L$ . One possible way to do this could be to write  $V_L$  as a function of  $R_L$ , differentiate this function with respect to  $R_L$ , and set the derivative to 0. Remember from calculus that the maxima and minima of functions are attained at those points where the derivative of the function is 0. Alternatively, you may also intuitively argue for a particular value of  $R_L$ . How does the voltage across a resistor change as the value of the resistor increases?)

- (b) Consider any value of  $R_L$  within the range:  $0 \leq R_L \leq \infty$ . Find the value of  $R_L$  that maximizes the **current**  $I_L$  through resistor  $R_L$ . Calculate the values of  $V_L$ ,  $I_L$ , and the power  $P_L$  dissipated by resistor  $R_L$  for the value you found.

(Hint: The antenna voltage  $V_S$  and the resistance  $R_S$  are fixed. However, you are free to choose the value of  $R_L$  in order to maximize the current  $I_L$ . One possible way of doing this is to write  $I_L$  as a function of  $R_L$ , differentiate this function with respect to  $R_L$ , and set the derivative to 0. Alternatively, you may also intuitively argue for a particular value of  $R_L$ .)

- (c) Find the value of  $R_L$  that maximizes the **power**  $P_L$  delivered to resistor  $R_L$ . Calculate the values of  $V_L$ ,  $I_L$ , and the power  $P_L$  delivered to resistor  $R_L$ . **It is important to note that this value of  $R_L$  which maximizes the power delivered to  $R_L$  also optimizes cellular connectivity.** (Hint: The power optimization is best performed algebraically by setting the derivative of  $P_L$  with respect to  $R_L$  to 0. Alternatively you can do the optimization graphically. Plot  $P_L$  versus  $R_L$  and find the maximum.)

### 3. Hot Dogs (Fa18, MT2)

(Contributors: Alice Ye, Michael Kellman, Urmita Sikder)

**Learning Goal:** The objective of this problem is to explore how power is dissipated in different resistors in series/parallel combination.

Michael and Alice are going on a picnic with Daisy the robot dog! But when they arrive at the park, a thunderstorm starts with lots of lightning... However, Daisy still wants to play in the park!

- (a) We want to understand what will happen *if* Daisy is struck by lightning. A lightning bolt is represented with a voltage source of 1000 Volts (1 kV) with reference to the Earth. The lightning travels through the ionized air ( $R_{Air} = 4\text{ k}\Omega$ ), and through Daisy ( $R_{Daisy} = 4\text{ k}\Omega$ ) before reaching the ground. Daisy can withstand up to 10 Watts (W) of power before breakdown, (i.e. Daisy will breakdown if she dissipates  $>10$  Watts).

Using the circuit diagram in Figure 1, find if it is safe for Daisy to be struck by a lightning bolt. Justify your answer by showing your work!

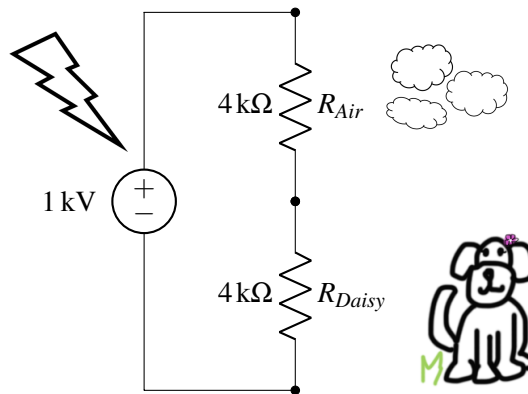


Figure 1: Circuit for Part (a)

- (b) Laura also brings along her dog, Elton, for the picnic. Elton has a resistance of  $R_{Elton} = 2\text{ k}\Omega$  and can withstand up to 25 W of power. If Daisy and Elton hide together next to a tree of resistance  $R_{Tree} = 4\text{ k}\Omega$  as shown in the Figure 2, would either of the dogs withstand being struck by lightning? Show your work.

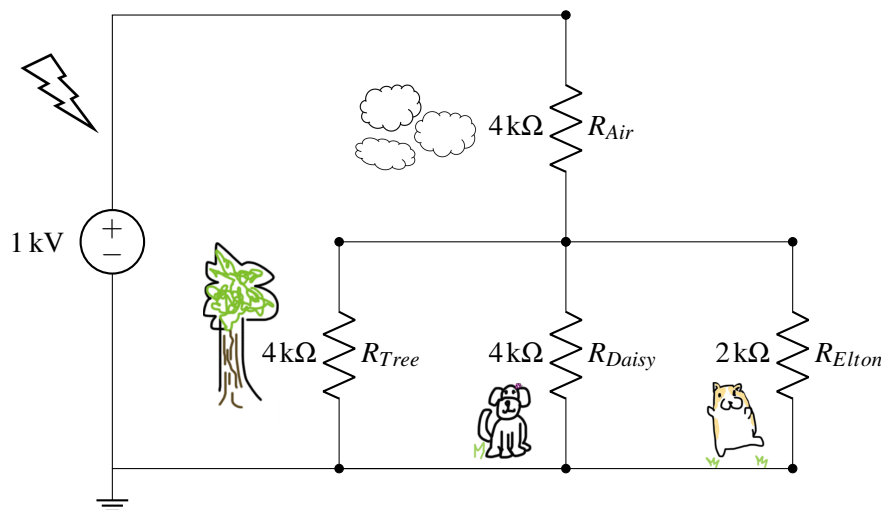



Figure 2: Circuit for Part (b)

#### 4. Equivalent Resistance


(Contributors: Craig Schindler, Panos Zarkos, Sashank Krishnamurthy, Urmita Sikder)

**Learning Goal:** The objective of this problem is to practice finding the equivalent to a series/parallel combination of resistors.

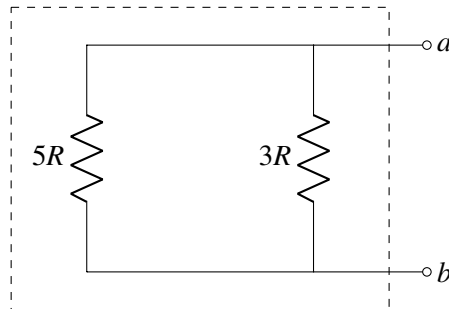
- (a) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



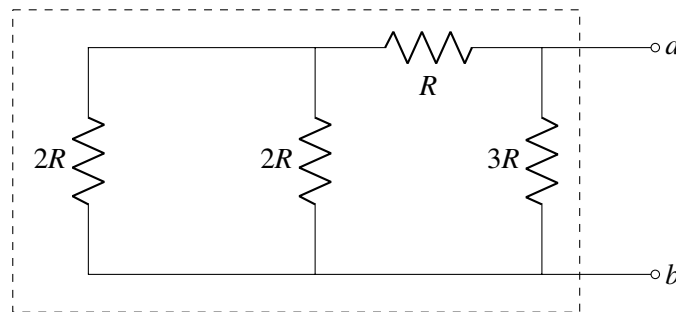
- (b) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



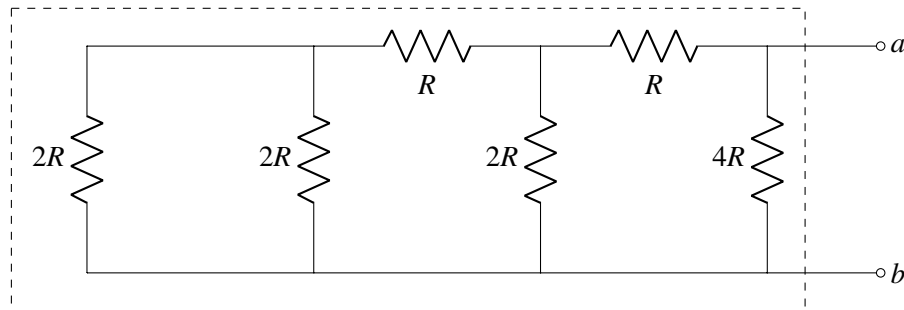
- (c) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



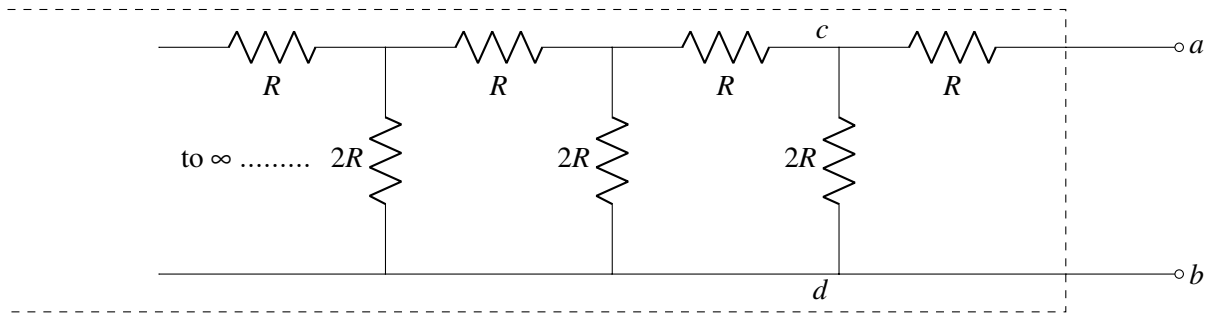- (d) **(OPTIONAL, CHALLENGE)** Find the equivalent resistance for the infinite ladder looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed region as one resistor. (Hint: Let's call the resistance looking in from  $a$  and  $b$  as  $R_{in}$ , and the resistance looking to the left from points  $c$  and  $d$  as  $R_{in1}$ . Replace the entire circuit to the left of points  $c$  and  $d$  with a resistor whose value is given by  $R_{in1}$ . Find the relationship between  $R_{in}$  and  $R_{in1}$  using this circuit. Find another relationship between  $R_{in}$  and  $R_{in1}$  using the fact that the ladder is infinite. For an infinite ladder, adding another branch does not change the equivalent resistance. Think of this as a convergent infinite series.)



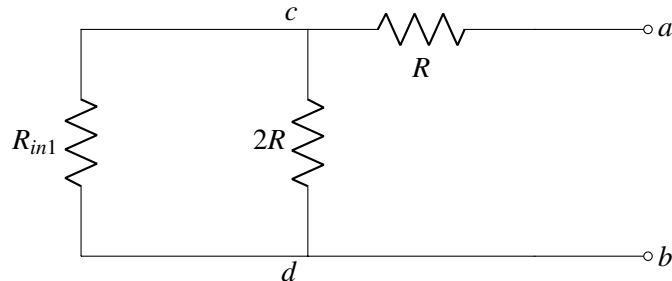As a first step you can replace the circuit looking to the left from  $c$  and  $d$  by  $R_{in1}$ .



### 5. Measuring Voltage and Current

(Contributors: Ava Tan, Aviral Pandey, Craig Schindler, Taehwan Kim, Urmita Sikder, Vijay Govindarajan, Wahid Rahman)

**Learning Goal:** The objective of this problem is to provide a deeper understanding in current and voltage measurement processes. It will also help you to understand how the electrical parameters of a measurement tool can affect the measurement precision.

In order to measure quantities such as voltage and current, engineers use voltmeters and ammeters. A simple model of a voltmeter is a resistor with a very high resistance,  $R_{VM}$ . **The voltmeter measures the voltage across the resistance  $R_{VM}$ .** The measured voltage is then relayed to a microprocessor (such as the MSP430 microprocessor, which will be used in lab).

This model of an voltmeter is shown in Figure 3. Let us explore what happens when we connect this voltmeter to various circuits to measure voltages.

Throughout this problem assume  $R_{VM} = 1M\Omega$ . Recall that the SI prefix M or Mega is  $10^6$ .

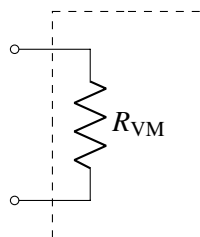


Figure 3: Our model of a voltmeter,  $R_{VM} = 1M\Omega$

- (a) Suppose we wanted to measure the voltage across  $R_2$  ( $v_{out}$ ) produced by the voltage divider circuit shown in Figure 4 on the left. The circuit on the right in Figure 4 shows how we would connect the

voltmeter across  $R_2$ . Assume  $R_1 = 100\Omega$  and  $R_2 = 200\Omega$ .

First calculate the value of  $v_{out}$ . Then calculate the voltage the voltmeter would measure, i.e.  $v_{meas}$ .

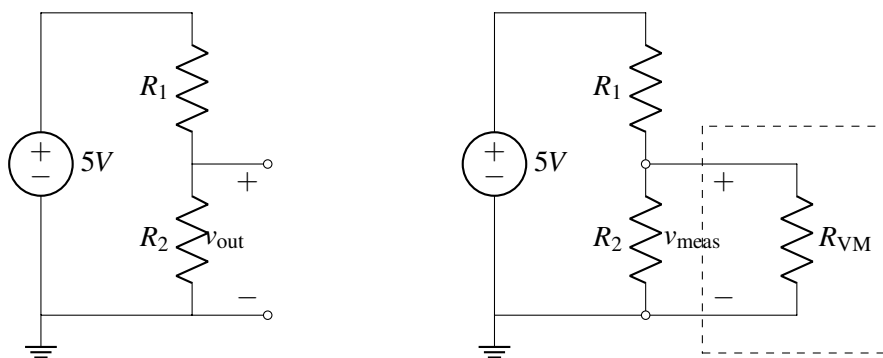


Figure 4: *Left*: Circuit without the voltmeter connected. *Right*: Voltmeter measuring voltage across  $R_2$ .

- (b) Repeat part (a), but now  $R_1 = 10M\Omega$  and  $R_2 = 10M\Omega$ . Is this particular voltmeter still a good tool to measure the output voltage? Justify why or why not. (Notice that a *good* voltmeter should not significantly affect the value of voltages in a circuit by its presence.)
- (c) Now suppose we are working with the same circuit as in part (a), but we know that  $R_2 = R_1$ . What is the maximum value of  $R_1$  such that  $v_{out} - v_{meas} \leq 0.1 \cdot v_{out}$  (i.e.  $v_{meas}$  is only 10% smaller than  $v_{out}$ )?
- (d) We can make **an ammeter** and measure the current through an element, using the combination of our voltmeter and an additional resistor  $R_x$ . The circuit shown in Figure 5 encompassed by the dashed box can work as an ammeter, where  $R_x = 1\Omega$ . We insert it in the circuit so that the current we want to measure flows through  $R_x$ , and then measure the current as  $I_{meas} = \frac{V_{VM}}{R_x}$  where  $V_{VM}$  is the voltage across the voltmeter.  $R_{VM} = 1M\Omega$  is the same as in previous parts.

In Figure 6, the voltmeter-resistor combo is connected so that the current we want to measure flows through resistor  $R_1 = 1k\Omega$ . For the circuit on the left, find the current through  $R_1$  without the voltmeter-resistor combo connected (i.e.  $I_1$ ). Then, for the circuit on the right, find the current measured by the voltmeter-resistor combo when it is connected as an ammeter (i.e.  $I_{meas}$ ).

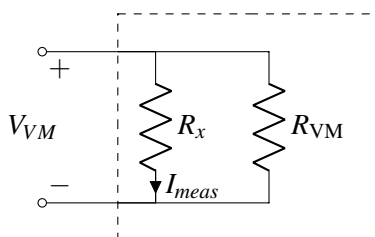


Figure 5: The voltmeter combined with resistor  $R_x$  to function as an ammeter (i.e. to measure current),  $R_{VM} = 1M\Omega$ .

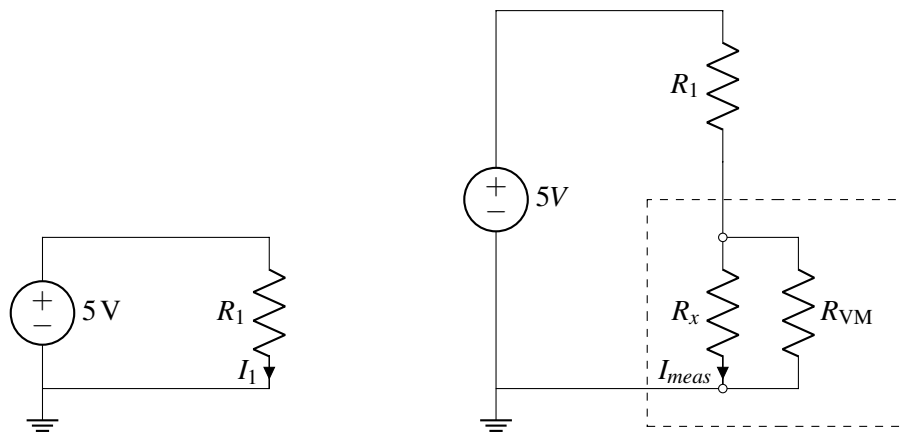


Figure 6: Circuits for part (d). *Left*: Original circuit; *Right*: Circuit with the voltmeter connected as an ammeter.

- (e) **(Optional)** What is the minimum value of  $R_1$  that ensures the difference between current measurement ( $I_{\text{meas}}$ ) and the the actual value ( $I_1$ ) is such that  $I_1 - I_{\text{meas}} \leq 0.1 \cdot I_1$ , i.e. stays within  $\pm 10\%$  of  $I_1$ ? In other words, find the minimum allowable value for  $R_1$  such that  $I_1 - I_{\text{meas}} \leq 0.1 \cdot I_1$ .


**Hint:** You can approximate  $R_{\text{VM}} \parallel R_x \approx R_x$  and  $\frac{R_{\text{VM}} \parallel R_x}{R_x} \approx 1$ .

## 6. Superposition

(Contributors: Avi Pandey, Gireeja Ranade, Karina Chang, Raghav Anand, Panos Zarkos, Sashank Krishnamurthy, Titan Yuan)

**Learning Goal:** The objective of this problem is to help you practice solving circuits using the principles of superposition.

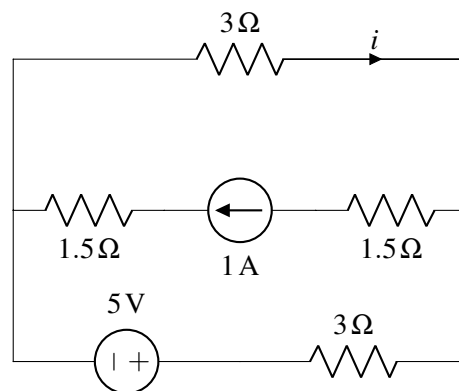Find the current  $i$  indicated in the circuit diagram below using superposition.



## 7. (Optional/Practice) Cell Phone Battery

(Contributors: Ava Tan, Aviral Pandey, Craig Schindler, Moses Won, Titan Yuan, Vijay Govindarajan, Wahid Rahman, Urmita Sikder)

**Learning Goal:** This problem explores how a battery can be modelled in a circuit. It also relates the concept of electric charge to current and energy.

As great as smartphones are, one of their drawbacks is that their batteries don't last a long time. For example, a Google Pixel phone, under typical usage conditions (internet, a few cat videos, etc.), **uses 0.3W**. We will **model the battery as an ideal voltage source** (which maintains a constant voltage across its terminals regardless of current) except that we assume that **the voltage drops abruptly to zero when the battery is discharged** (in reality the voltage drops gradually, but let's keep things simple).

Battery capacity is specified in mAh, which indicates how many mA of current the battery can supply for one hour before it needs to be recharged. The Pixel's battery has a battery capacity of 2770mAh at 3.8V. For example, this battery could provide 1000mA (or 3.8W) for 2.77 hours before the voltage abruptly drops from 3.8V to zero.

- How long will a Pixel's full battery last under typical usage conditions? Remember that under typical usage conditions it uses 0.3W.
- How many coulombs of charge does the battery contain? How many usable electrons worth of charge are contained in the battery when it is fully charged? (An electron has  $1.602 \times 10^{-19}$  C of charge.)
- Suppose the cell phone battery is completely discharged and you want to recharge it completely. How much energy (in J) is this? Recall that a J is equivalent to a W s.
- Suppose PG&E charges \$0.12 per kWh. Every day, you completely discharge the battery (meaning more than typical usage) and you recharge it every night. How much will recharging cost you for the month of October (31 days)?
- The battery has internal circuitry that prevents it from getting overcharged (and possibly exploding!). We will model the battery and its internal circuitry as a resistor  $R_{\text{bat}}$ . We now wish to charge the battery by plugging into a wall plug. The wall plug can be modeled as a 5V voltage source and 200 m $\Omega$  resistor, as pictured in Figure 7.

What is the power dissipated by  $R_{\text{bat}}$  for  $R_{\text{bat}} = 1 \text{ m}\Omega$ ,  $1 \Omega$ , and  $10 \text{ k}\Omega$ , i.e. how much power is being supplied to the phone battery as it is charging? How long will the battery take to charge for each value of  $R_{\text{bat}}$ ?

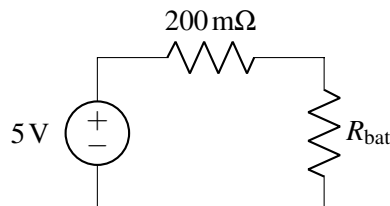


Figure 7: Model of wall plug, wire, and battery.

## 8. Mid-semester Class Survey

Please fill out the EECS16A Mid-semester Class Survey ([click here](#)). We appreciate your feedback towards improving this class — this really helps us improve future semesters as well as latter parts of this class. This survey is completely anonymous.

**An incentive to do this: If more than 75% of the class fills out this survey in full, we will add 1 point to everyone's MT1 score. If more than 85% of the class fills out this survey in full, we will add 2 points to everyone's MT1 score.**

Note: If you would like to request a new study group, you may fill out the following survey: <https://tinyurl.com/reassign-16a-1>



## **9. Homework Process and Study Group**

Who did you work with on this homework? List names and student ID's. (In case you met people at homework party or in office hours, you can also just describe the group.) How did you work on this homework? If you worked in your study group, explain what role each student played for the meetings this week.